

Analog to Digital Converter

What is ADC ?

Types of ADCs

Denis BISSIERES

Ian CAMPBELL

Yohan LESPERAT



Contents

- What is ADC ?
- Types of ADCs

What is ADC ?

Types of ADCs

What is ADC ?

- Definition
- Examples of use
- Conversion process
- Accuracy


What is ADC ?

Types of ADCs

HC11 & ADC

Definition

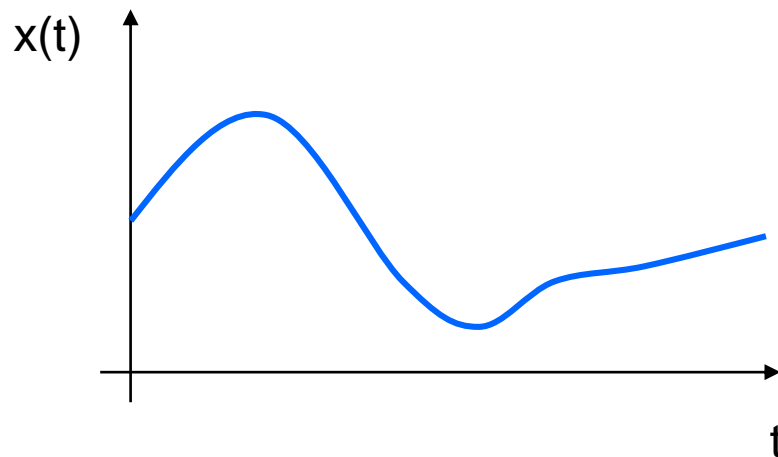- Most signals we want to process are analog
- i.e.: they are continuous and can take an infinity of values




What is ADC ?

Types of ADCs

HC11 & ADC

Definition

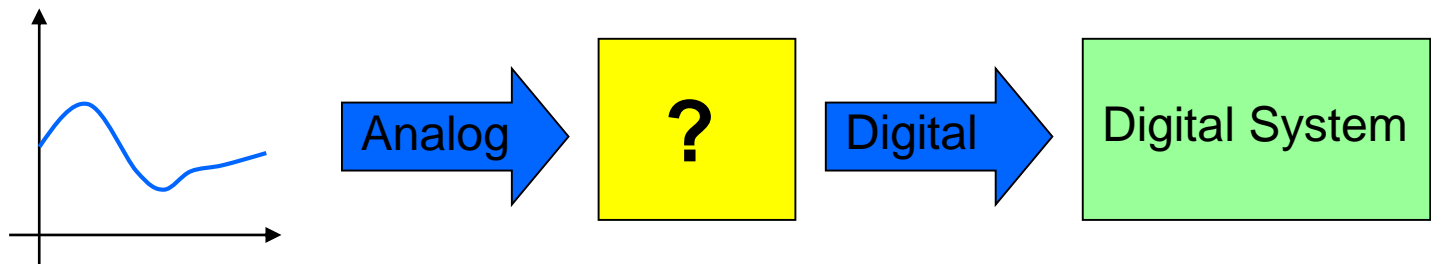- Digital systems require discrete digital data
- ADC converts an analog information into a digital information




What is ADC ?

Types of ADCs


HC11 & ADC

Examples of use

- Voltmeter

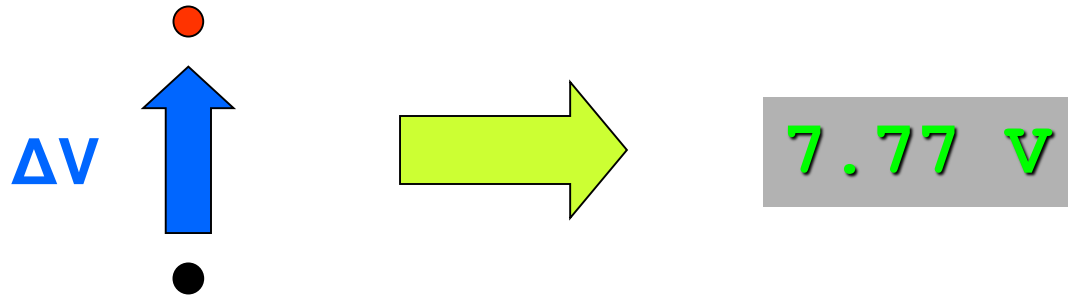

- Cell phone (microphone)

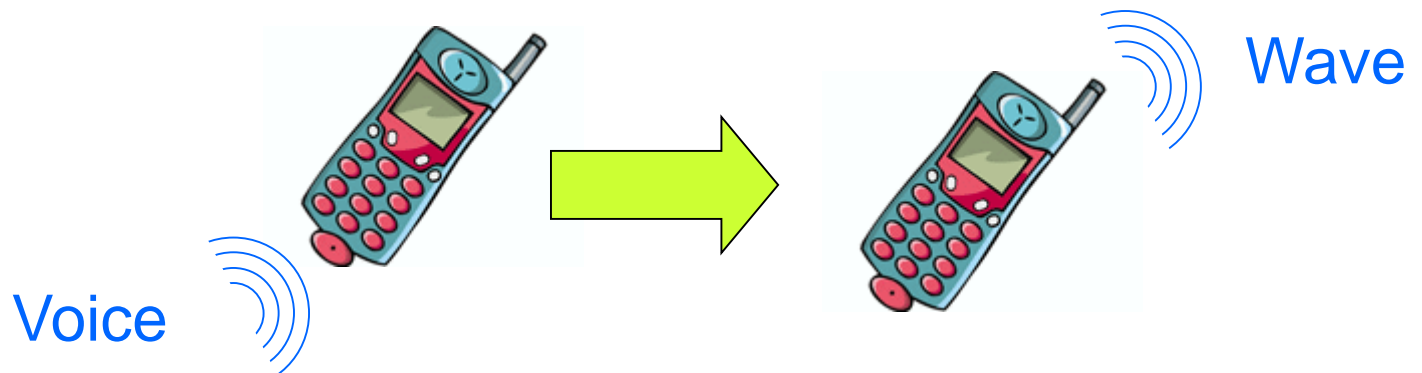

What is ADC ?

Types of ADCs

HC11 & ADC

Conversion process

3 steps:

- Sampling
- Quantification
- Coding

These operations are all performed in a same element: **the A to D Converter**


What is ADC ?

Types of ADCs

HC11 & ADC

Conversion process: Sampling

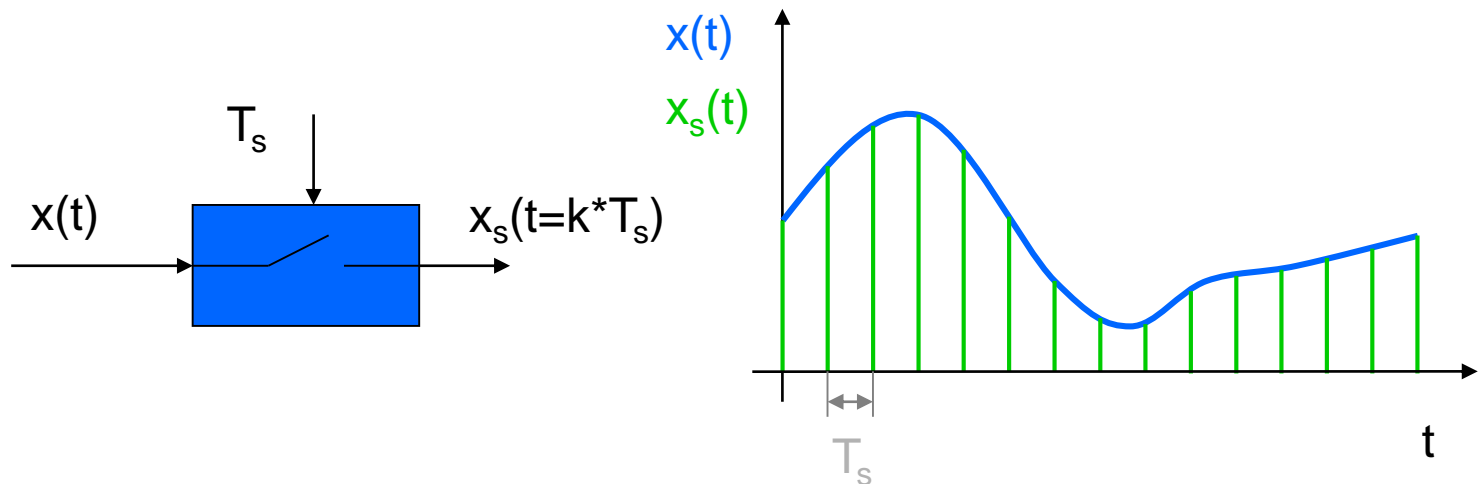- Digital system works with discrete states
- The signal is only defined at determined times
- The sampling times are proportional to the sampling period (T_s)



What is ADC ?

Types of ADCs


HC11 & ADC

Conversion process: Quantification

The signal can only take determined values

Belonging to a range of conversion (ΔV_r)

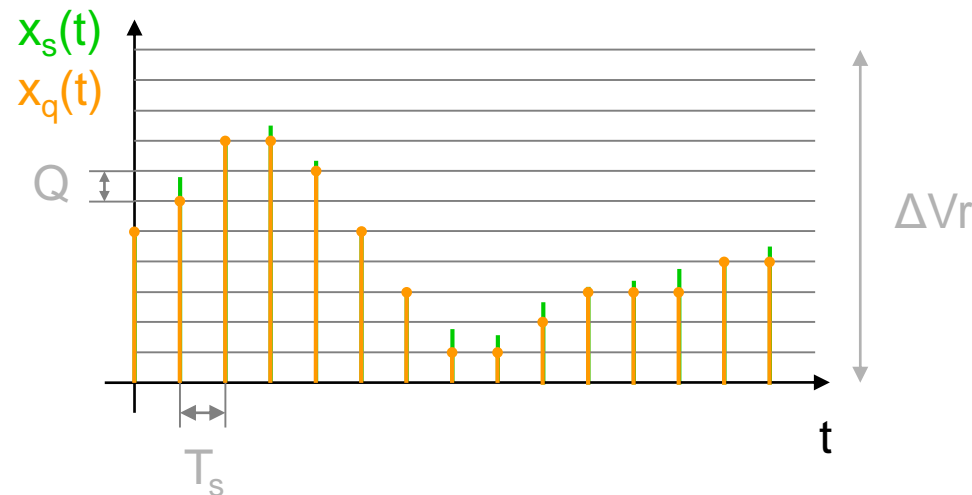- Based on number of bit combinations that the converter can output
- Number of possible states:
 $N=2^n$ where n is number of bits
- Resolution: $Q= \Delta V_r/N$




What is ADC ?

Types of ADCs

HC11 & ADC

Conversion process: Coding

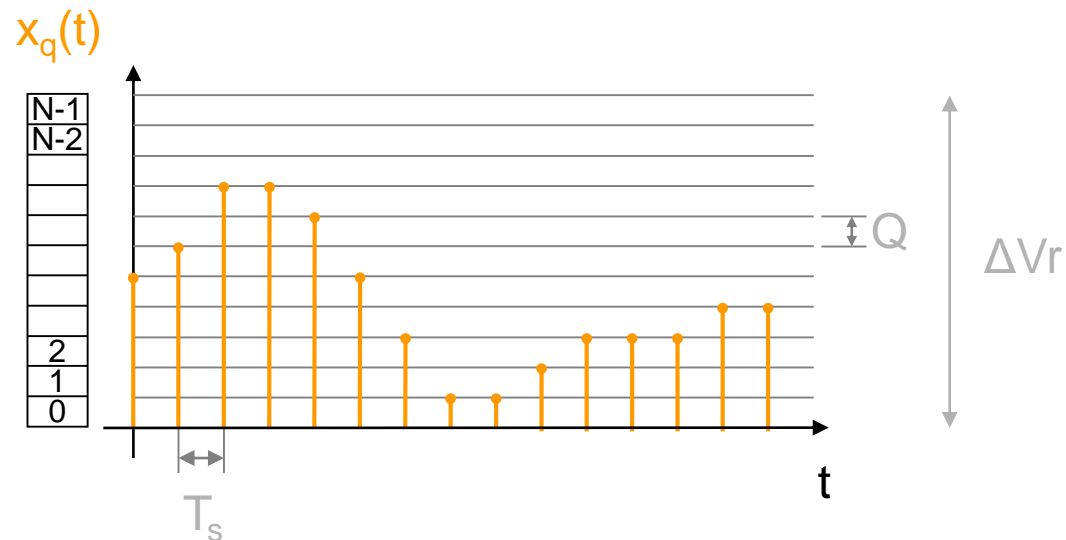- Assigning a unique digital word to each sample
- Matching the digital word to the input signal



What is ADC ?

Types of ADCs

HC11 & ADC

Accuracy

The accuracy of an ADC can be improved by increasing:


- The sampling rate (T_s)
- The resolution (Q)

What is ADC ?


Types of ADCs

HC11 & ADC


Accuracy

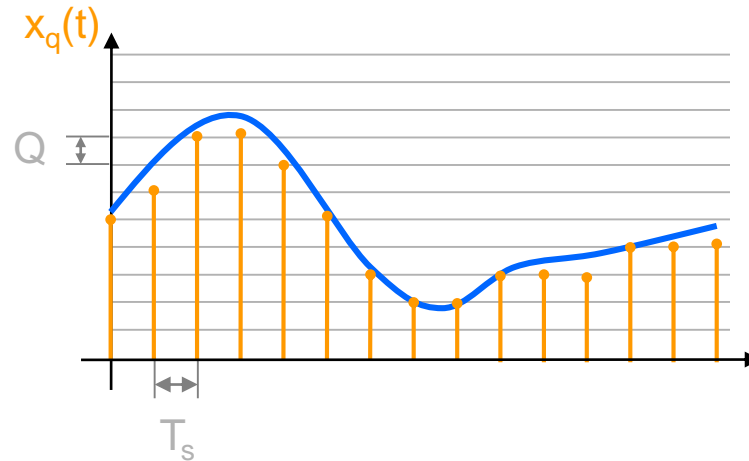

Higher Sampling rate

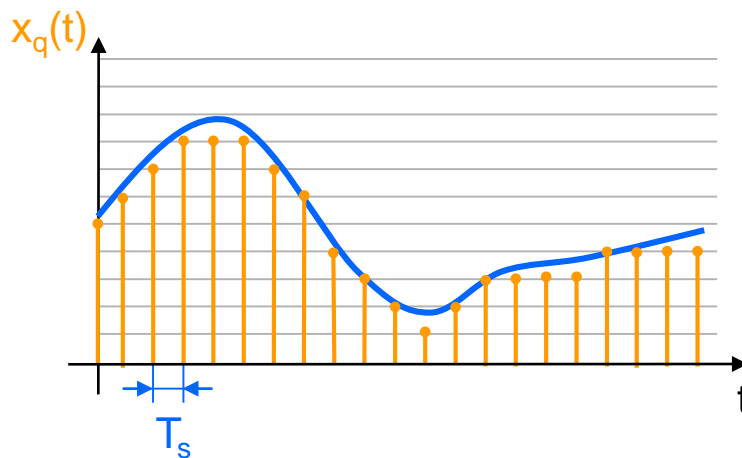

Higher Resolution

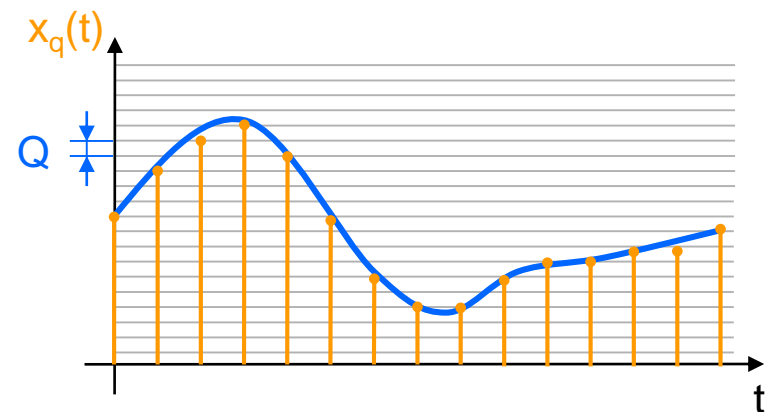

What is ADC ?


Types of ADCs

HC11 & ADC

Sampling rate

Nyquist-Shannon theorem: Minimum sampling rate should be at least twice the highest data frequency of the analog signal

$$f_s > 2 * f_{\max}$$

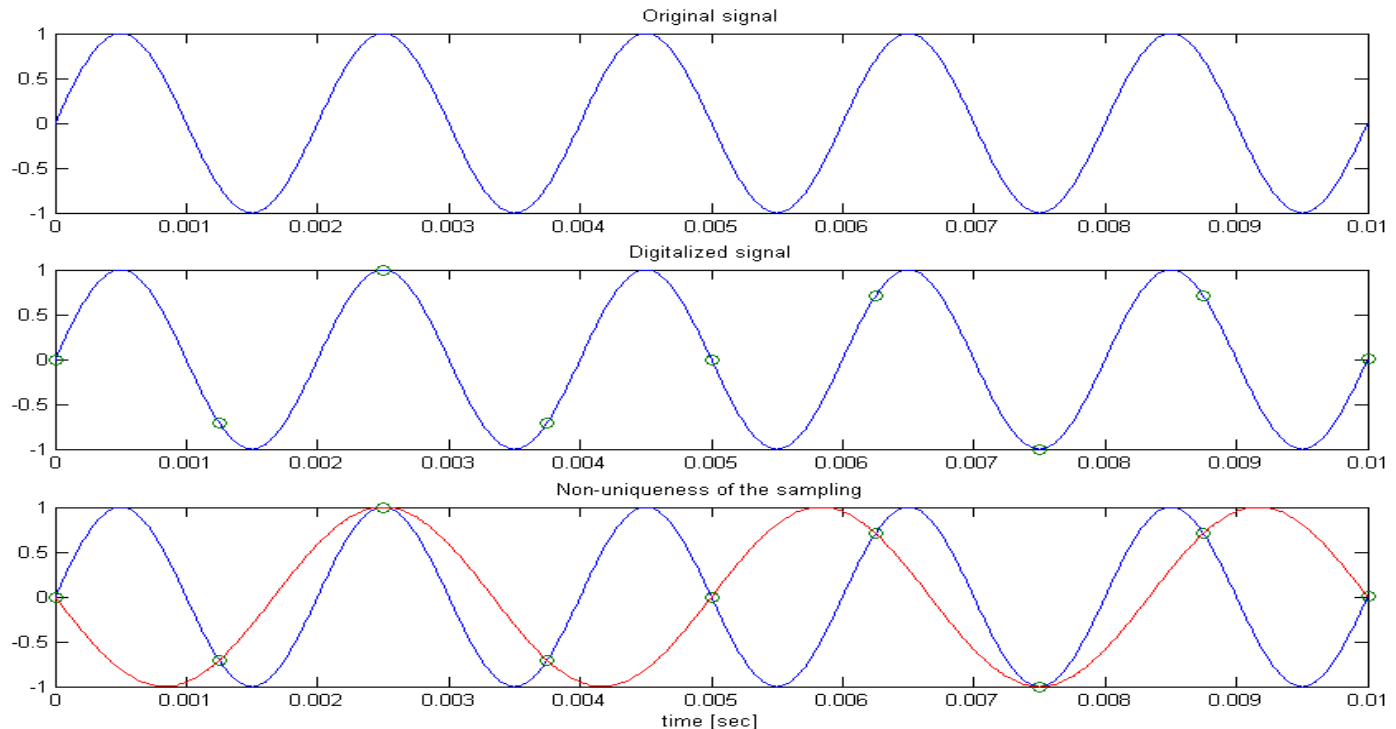


What is ADC ?

Types of ADCs

HC11 & ADC

Sampling rate

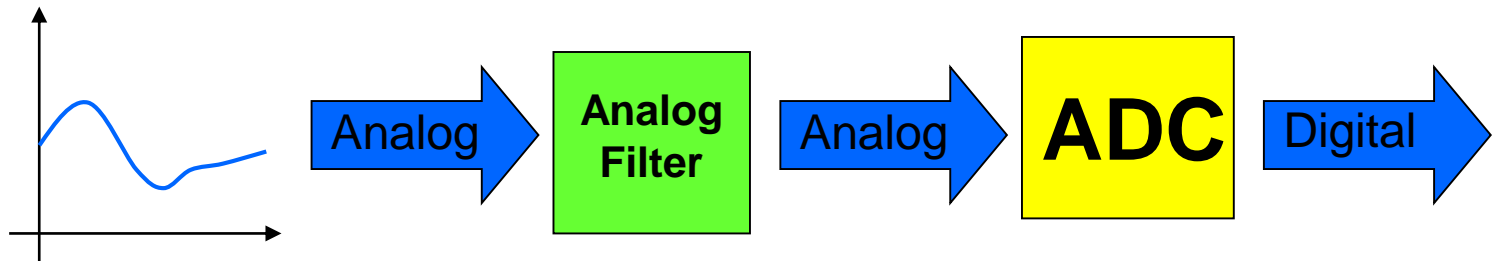- Analog signals are composed of an infinity of harmonics
- Need to limit the frequency band to its useful part
- Use of an analog filter



In practice: $f_s \approx (3 \dots 5) \cdot f_{\text{filter}}$

What is ADC ?



Types of ADCs

HC11 & ADC

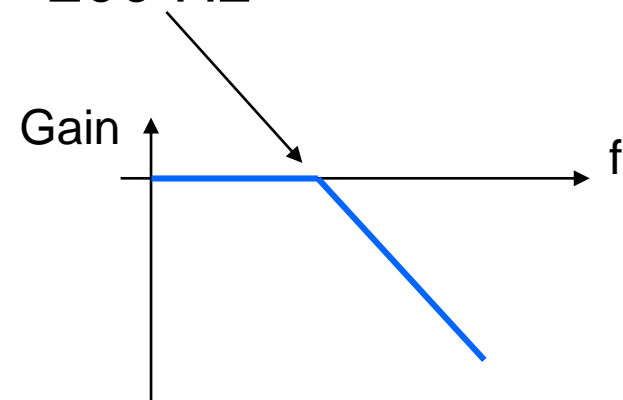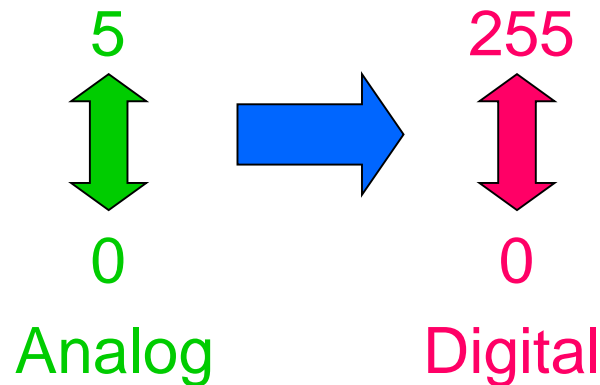Example

- 8 bits converter: $n=8$
- Range of conversion: $\Delta V_r=5V$
- Sampling time: $T_s=1ms$

- Number of possible states: $N=2^8=256$
- Resolution: $Q=\Delta V_r/N=19.5\text{ mV}$
- Analog Filter: $f_{\text{filter}} \approx f_s/5 = 200\text{ Hz}$



Types of ADCs


- Flash ADC
- Sigma-delta ADC
- Dual slope converter
- Successive approximation converter

What is ADC ?

Types of ADCs

HC11 & ADC

Flash ADC

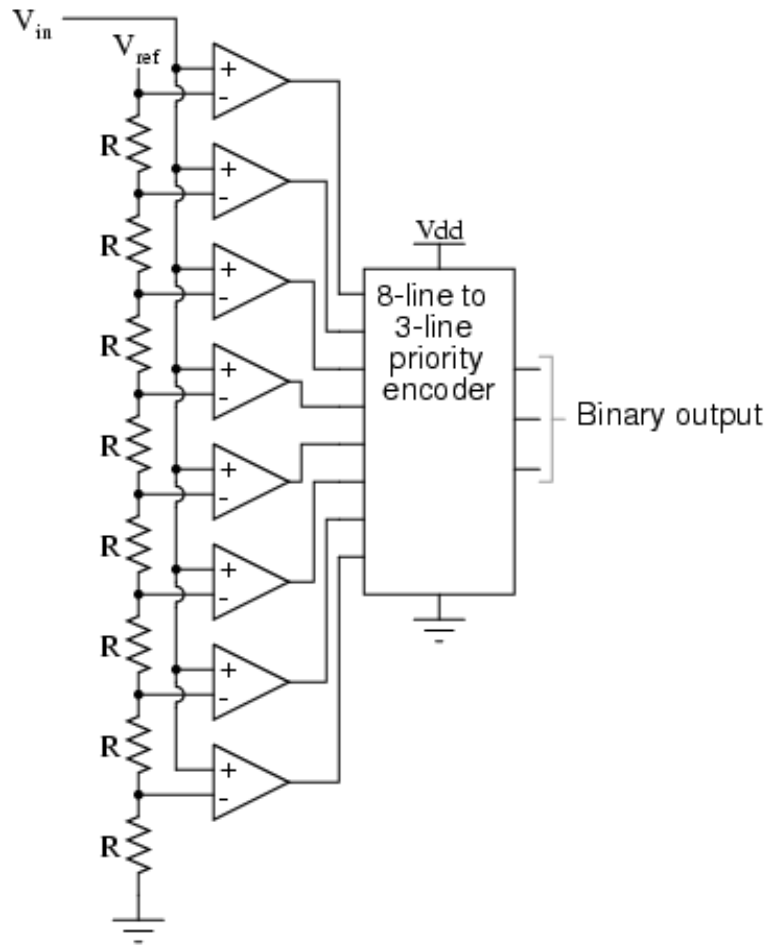

- “parallel A/D”
- Uses a series of comparators
- Each comparator compares V_{in} to a different reference voltage, starting w/ $V_{ref} = 1/2 \text{ lsb}$


What is ADC ?

Types of ADCs

HC11 & ADC

Flash ADC

Comparator is one use
of an Op-Amp

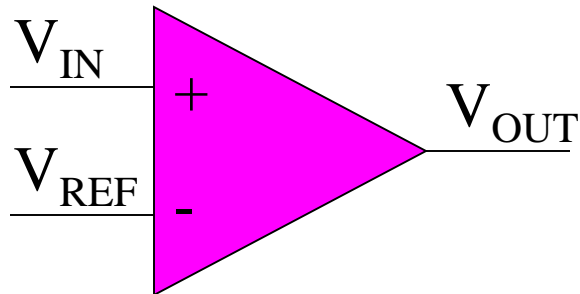

If	Output
$V_{IN} > V_{REF}$	High
$V_{IN} < V_{REF}$	Low

What is ADC ?

Types of ADCs

HC11 & ADC

Flash ADC

Advantages

- Very fast

Disadvantages


- Needs many parts (255 comparators for 8-bit ADC)
- Lower resolution
- Expensive
- Large power consumption

What is ADC ?

Types of ADCs

HC11 & ADC

Sigma-Delta ADC

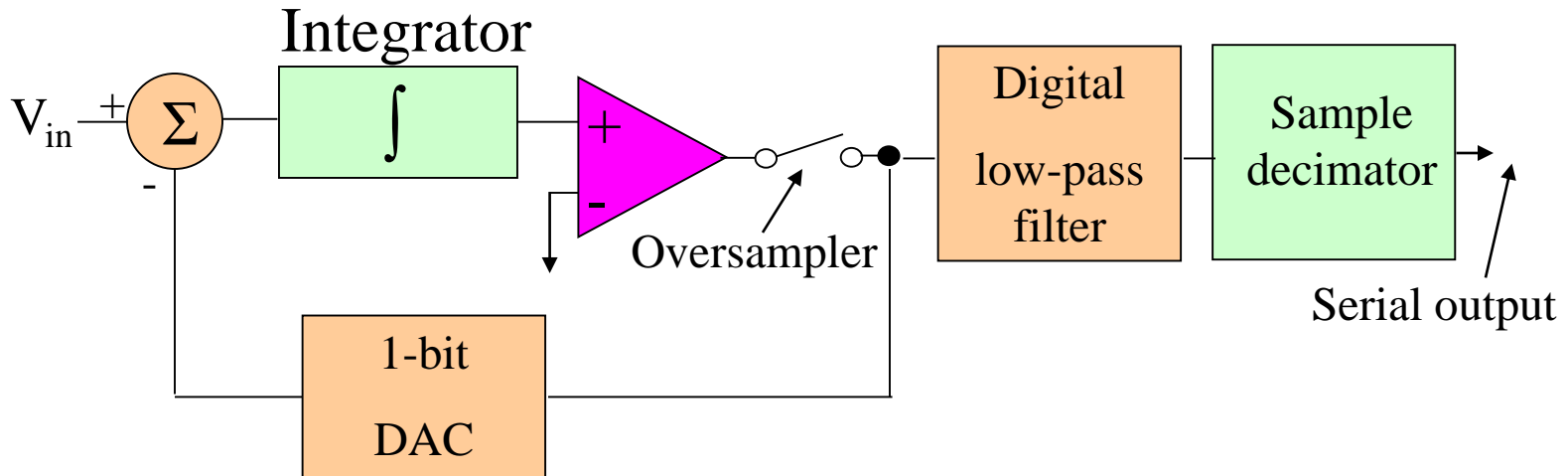

- Oversampled input signal goes in the integrator
- Output of integration is compared to GND
- Iterates to produce a serial bitstream
- Output is serial bit stream with # of 1's proportional to V_{in}

What is ADC ?

Types of ADCs

HC11 & ADC

Sigma-Delta ADC

Advantages

- High resolution
- No precision external components needed

Disadvantages


- Slow due to oversampling

What is ADC ?

Types of ADCs

HC11 & ADC

Dual Slope converter

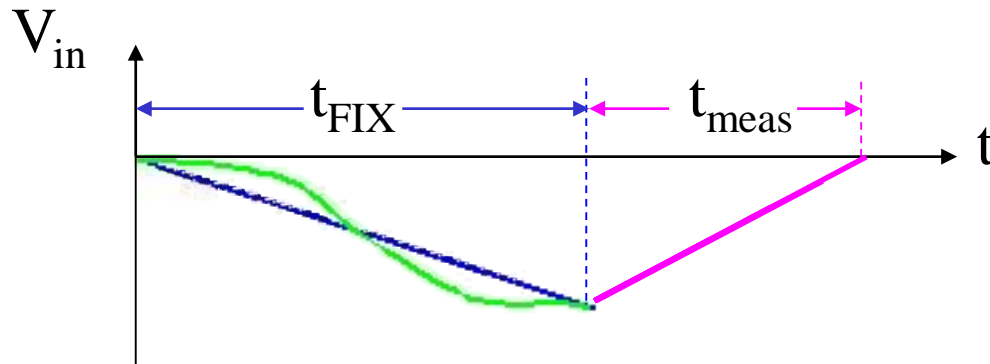

- The sampled signal charges a capacitor for a fixed amount of time
- By integrating over time, noise integrates out of the conversion.
- Then the ADC discharges the capacitor at a fixed rate while a counter counts the ADC's output bits. A longer discharge time results in a higher count.

What is ADC ?

Types of ADCs

HC11 & ADC

Dual Slope converter

Advantages

- Input signal is averaged
- Greater noise immunity than other ADC types
- High accuracy

Disadvantages

- Slow
- High precision external components required to achieve accuracy


What is ADC ?

Types of ADCs


HC11 & ADC

Successive Approximation

Is $V_{in} > \frac{1}{2}$ ADC range?

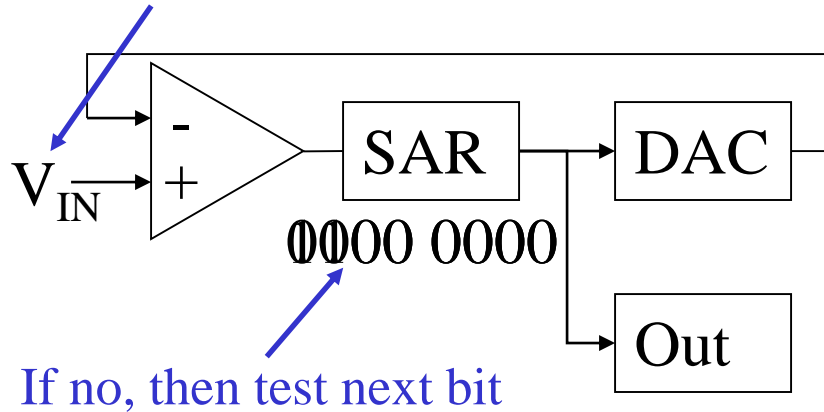

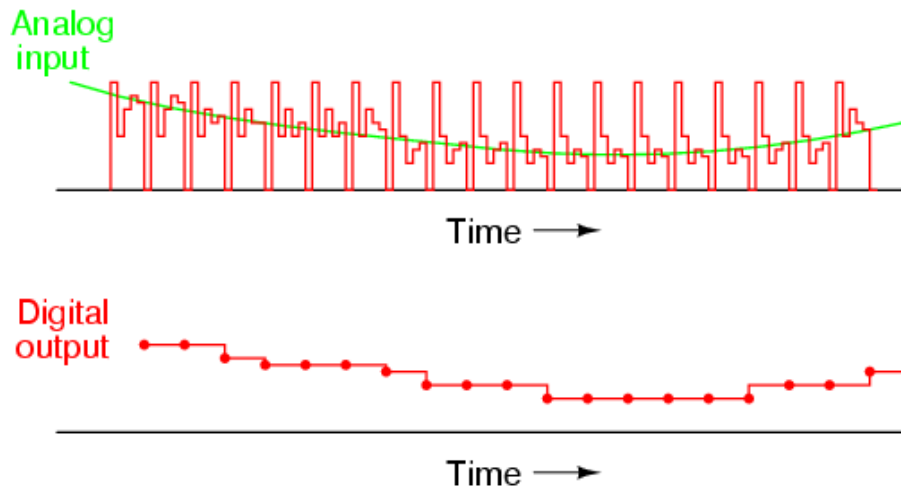- Sets MSB
- Converts MSB to analog using DAC
- Compares guess to input
- Set bit
- Test next bit



What is ADC ?

Types of ADCs

HC11 & ADC

Successive Approximation

Advantages

- Capable of high speed
- Medium accuracy compared to other ADC types
- Good tradeoff between speed and cost

Disadvantages

- Higher resolution successive approximation ADCs will be slower
- Speed limited
~5Msps


What is ADC ?

Types of ADCs

HC11 & ADC

ADC Types Comparison

ADC Resolution Comparison

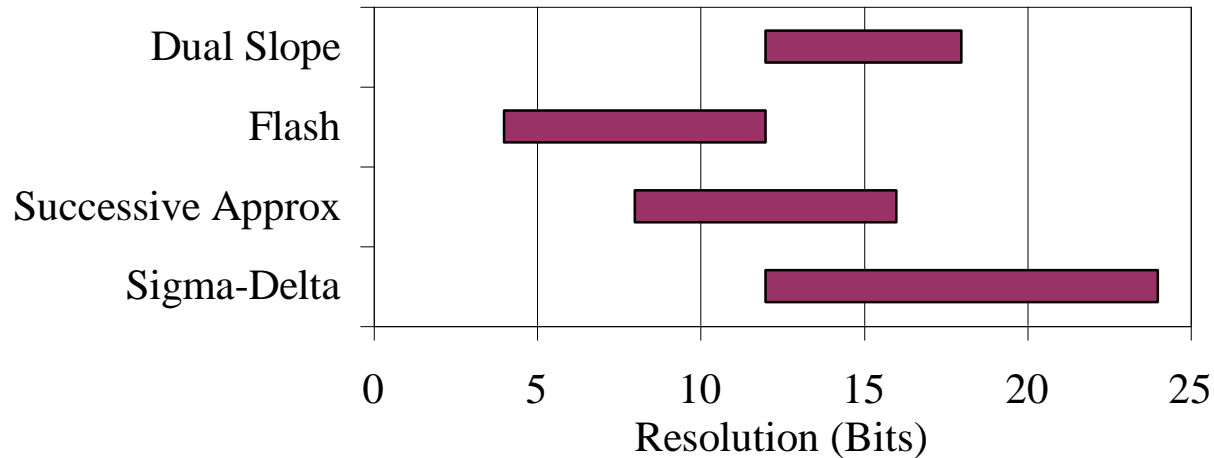

Type	Speed (relative)	Cost (relative)
Dual Slope	Slow	Med
Flash	Very Fast	High
Successive Appox	Medium – Fast	Low
Sigma-Delta	Slow	Low

What is ADC ?

Types of ADCs