



Digital to Analog Converters (DAC)




Outline

- Purpose
- Types
- Performance Characteristics
- Applications

Purpose

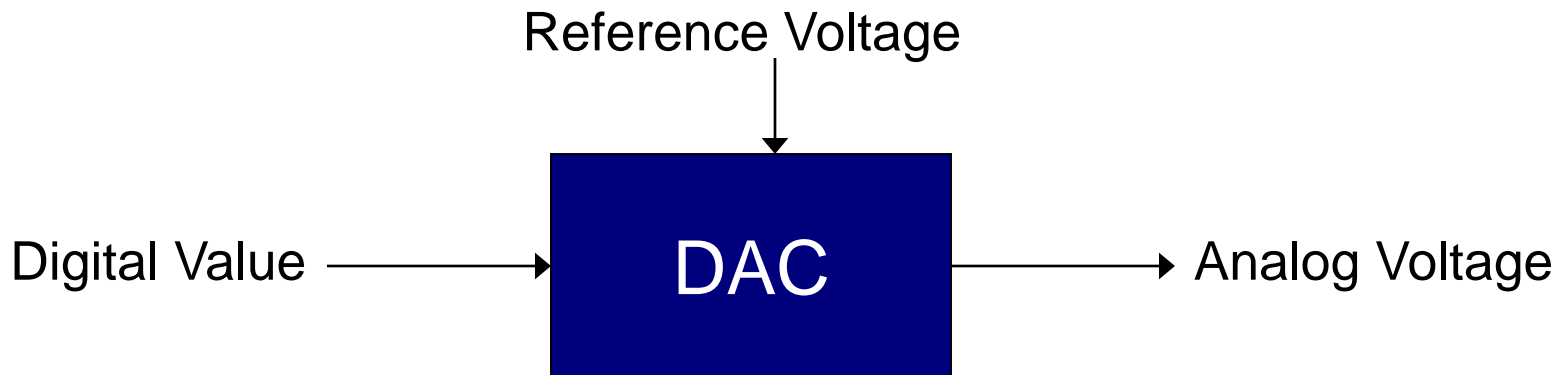- To convert digital values to analog voltages
- Performs inverse operation of the Analog-to-Digital Converter (ADC)
- $V_{OUT} \propto \text{Digital Value}$



DACs


■ Types

- ☐ Binary Weighted Resistor
- ☐ R-2R Ladder
- ☐ Multiplier DAC
 - The reference voltage is constant and is set by the manufacturer.
- ☐ Non-Multiplier DAC
 - The reference voltage can be changed during operation.


■ Characteristics

- ☐ Comprised of switches, op-amps, and resistors
- ☐ Provides resistance inversely proportion to significance of bit


Binary Weighted Resistor

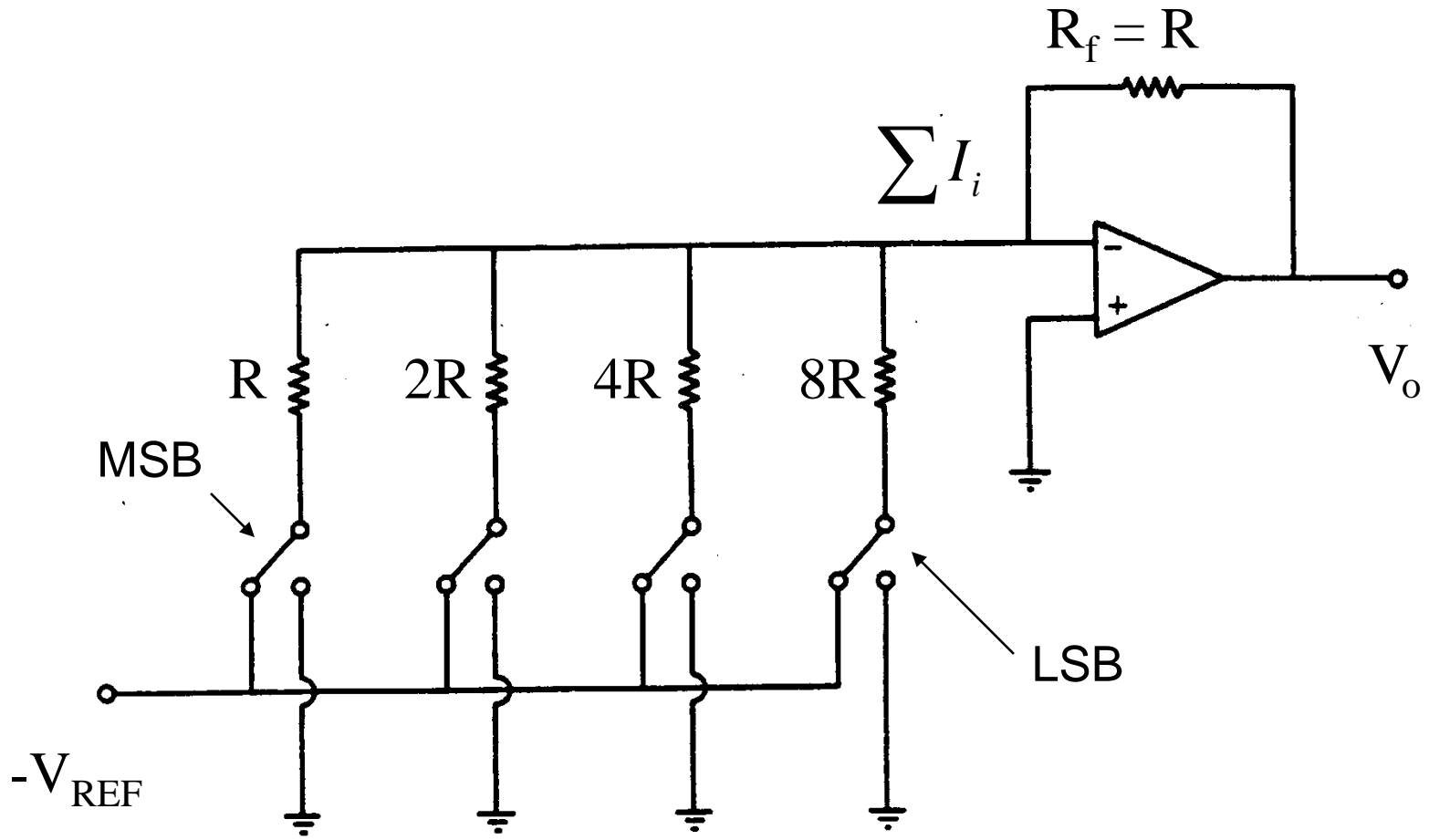

Binary Representation

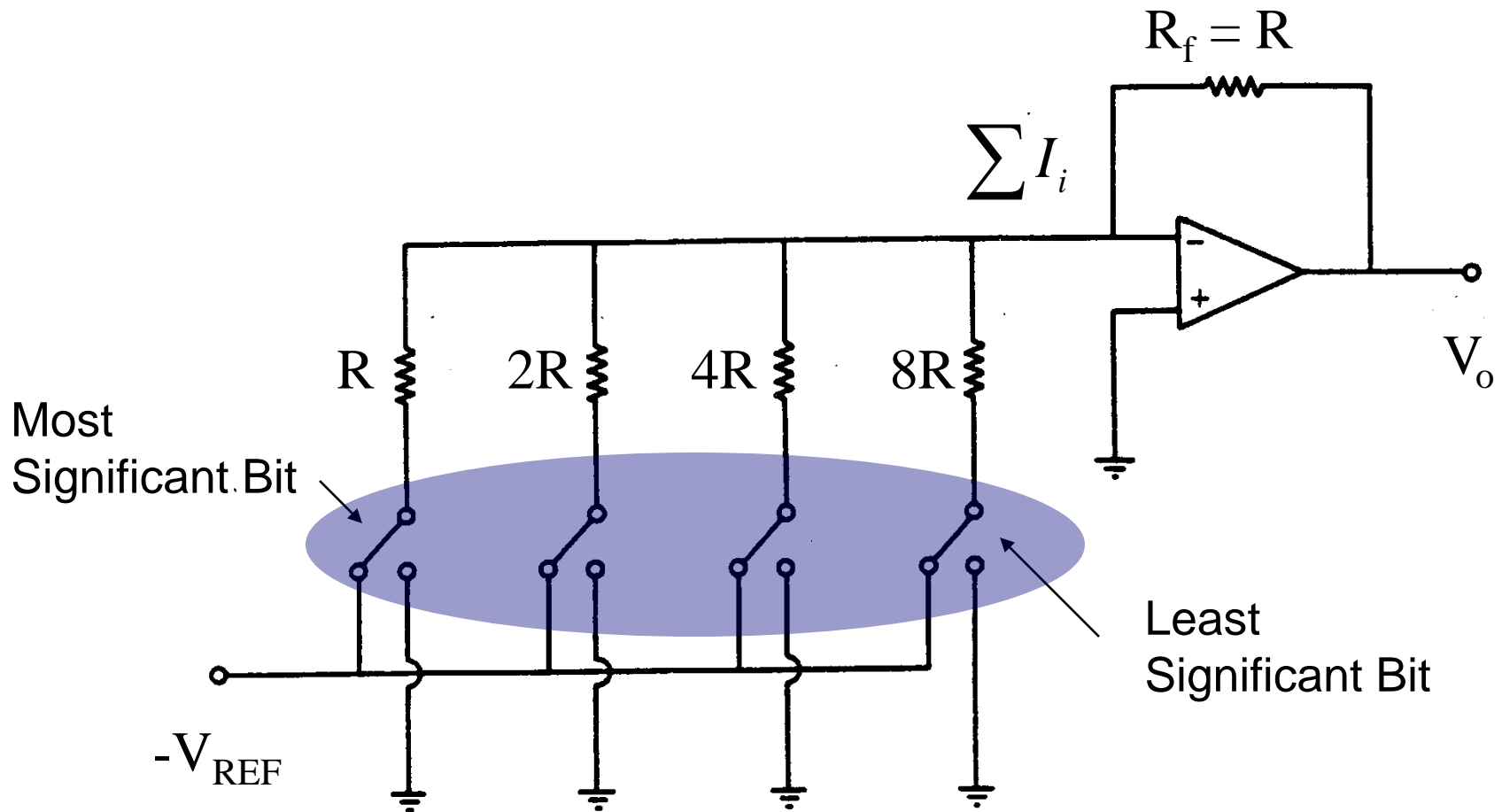


Binary Representation

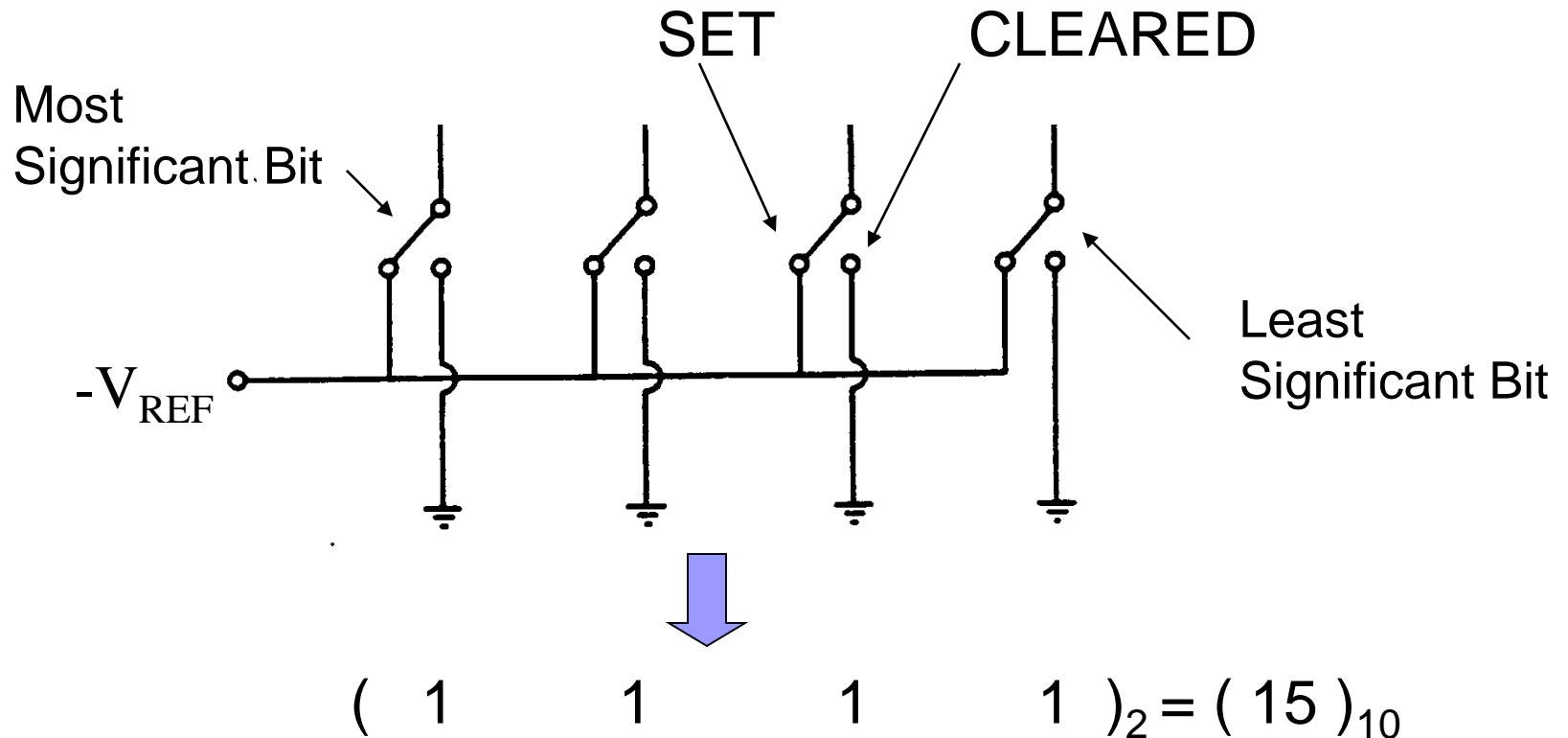

Binary Weighted Resistor

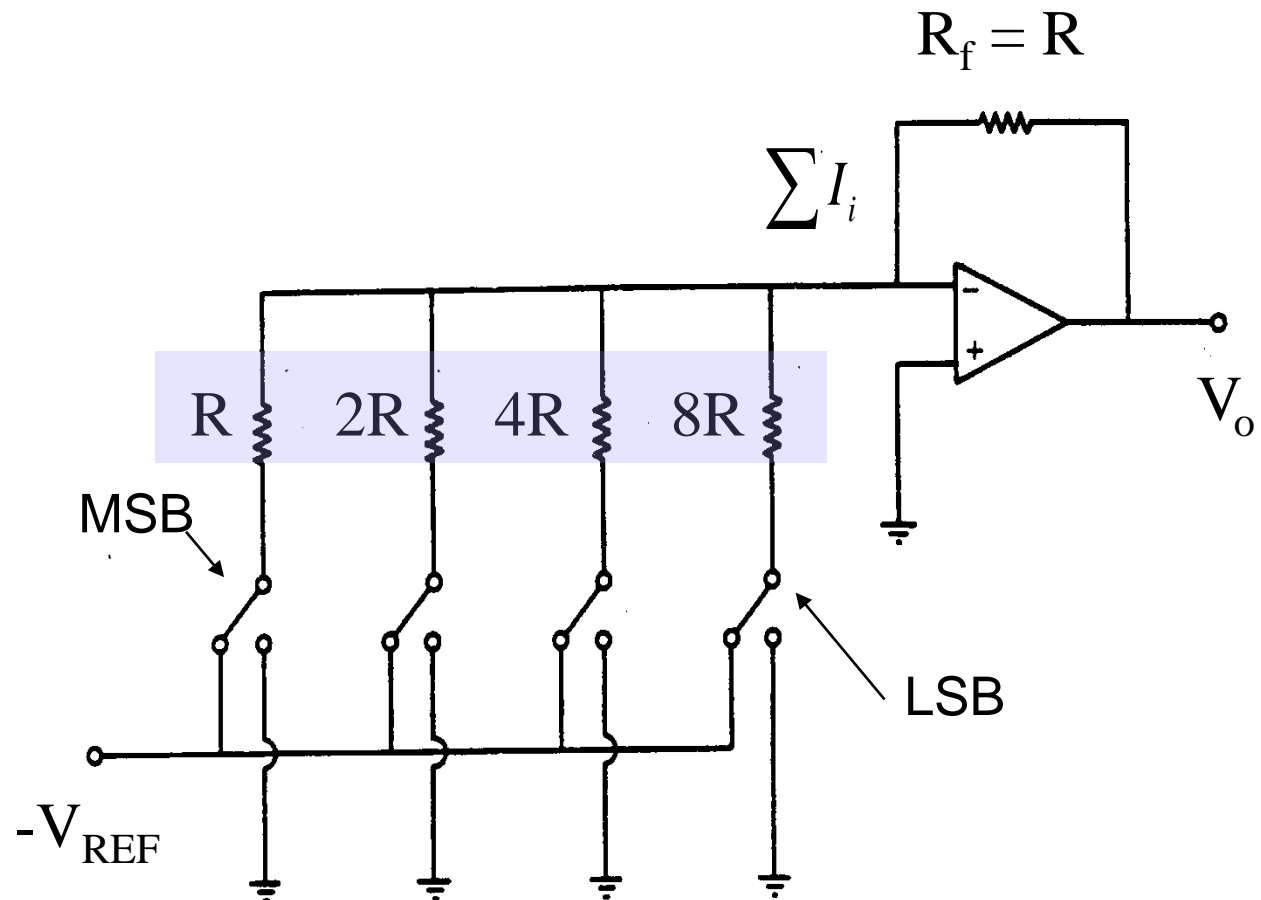- “Weighted Resistors” based on bit
- Reduces current by a factor of 2 for each bit



Binary Weighted Resistor

- Result:

$$\sum I = V_{REF} \left(\frac{B_3}{R} + \frac{B_2}{2R} + \frac{B_1}{4R} + \frac{B_0}{8R} \right)$$

$$V_{OUT} = I \cdot R_f = V_{REF} \left(B_3 + \frac{B_2}{2} + \frac{B_1}{4} + \frac{B_0}{8} \right)$$

□ B_i = Value of Bit i


Binary Weighted Resistor

- More Generally:

$$\begin{aligned} V_{OUT} &= V_{REF} \sum \frac{B_i}{2^{n-i-1}} \\ &= V_{REF} \cdot \text{Digital Value} \cdot \text{Resolution} \end{aligned}$$


- B_i = Value of Bit i
- n = Number of Bits

R-2R Ladder

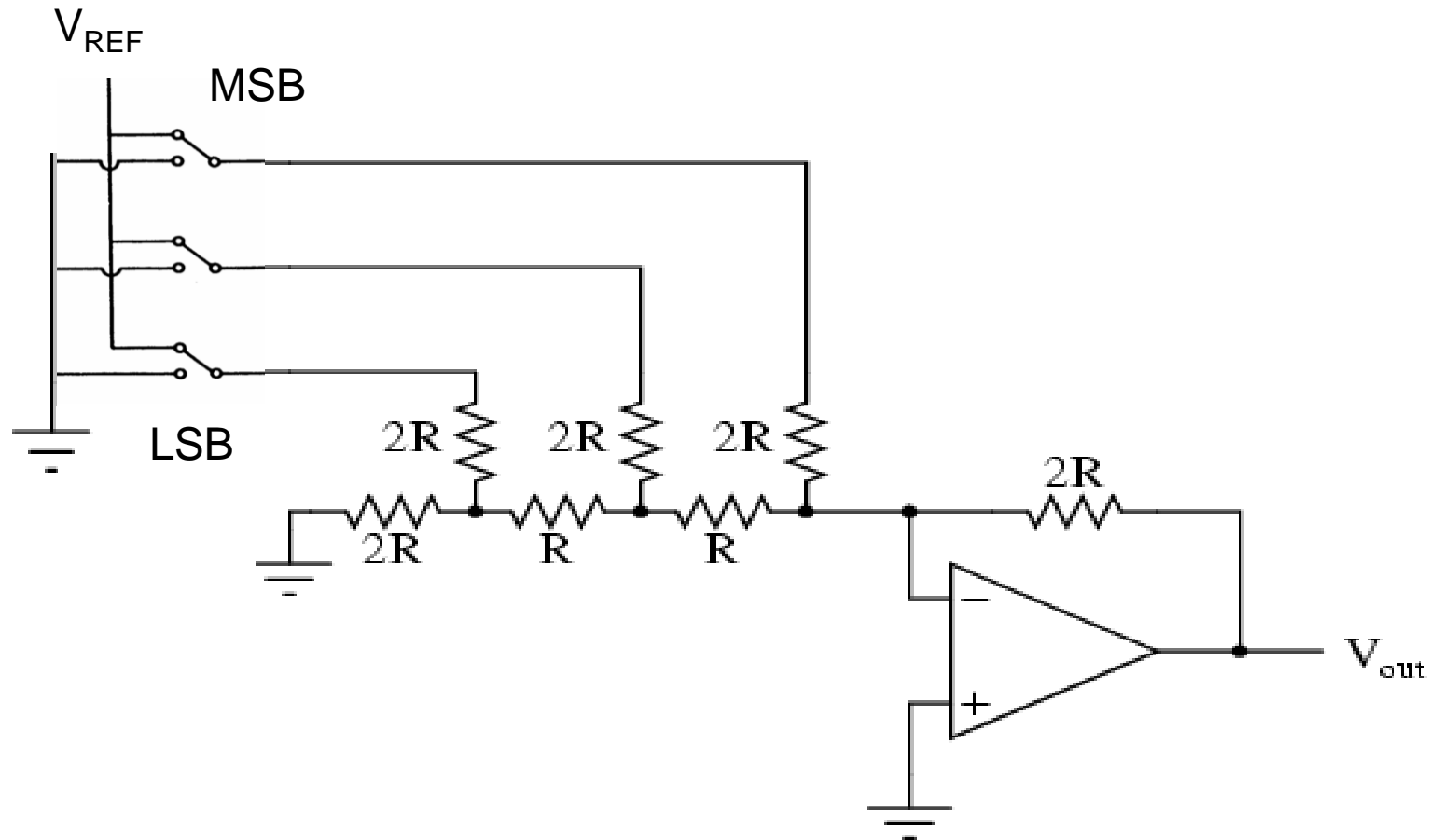


R-2R Ladder

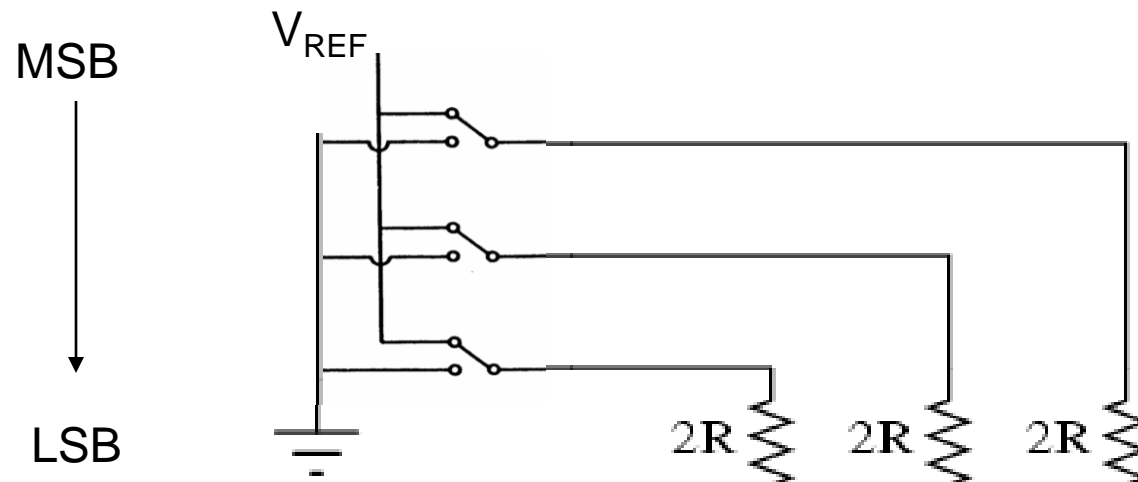- Same input switch setup as Binary Weighted Resistor DAC
- All bits pass through resistance of $2R$




R-2R Ladder

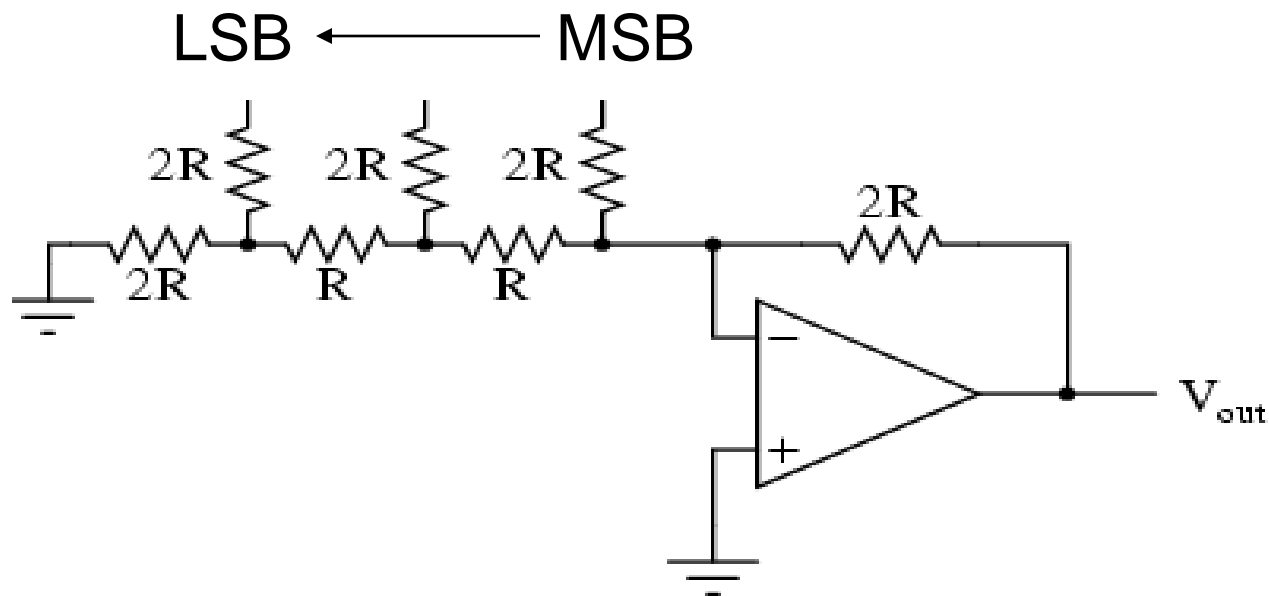- The less significant the bit, the more resistors the signal must pass through before reaching the op-amp
- The current is divided by a factor of 2 at each node



R-2R Ladder

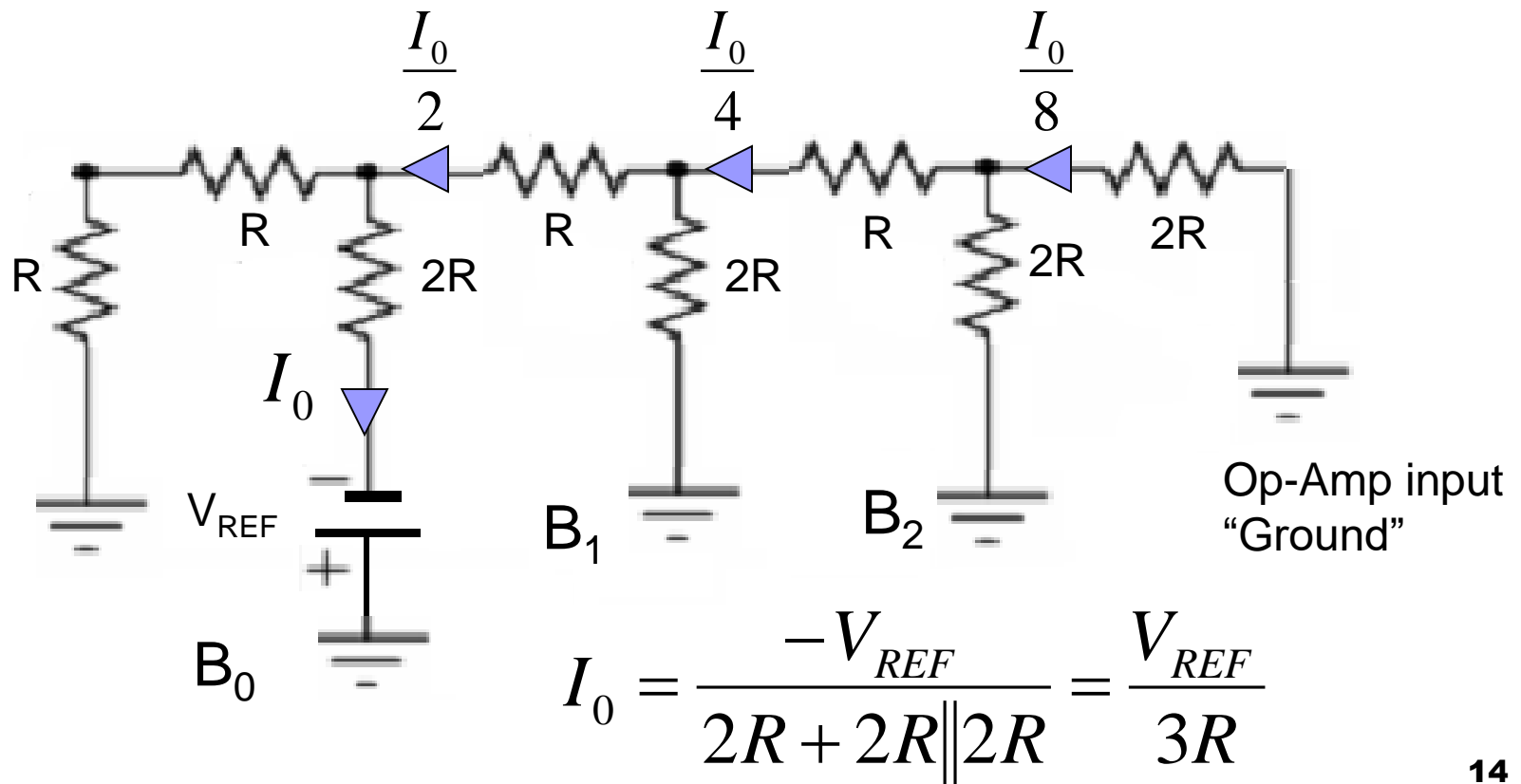- The current is divided by a factor of 2 at each node
- Analysis for current from $(001)_2$ shown below




R-2R Ladder

■ Result:

$$I = \frac{V_{REF}}{3R} \left(\frac{B_2}{2} + \frac{B_1}{4} + \frac{B_0}{8} \right)$$

$$V_{OUT} = \frac{R_f}{R} V_{REF} \left(\frac{B_2}{2} + \frac{B_1}{4} + \frac{B_0}{8} \right)$$

□ B_i = Value of Bit i

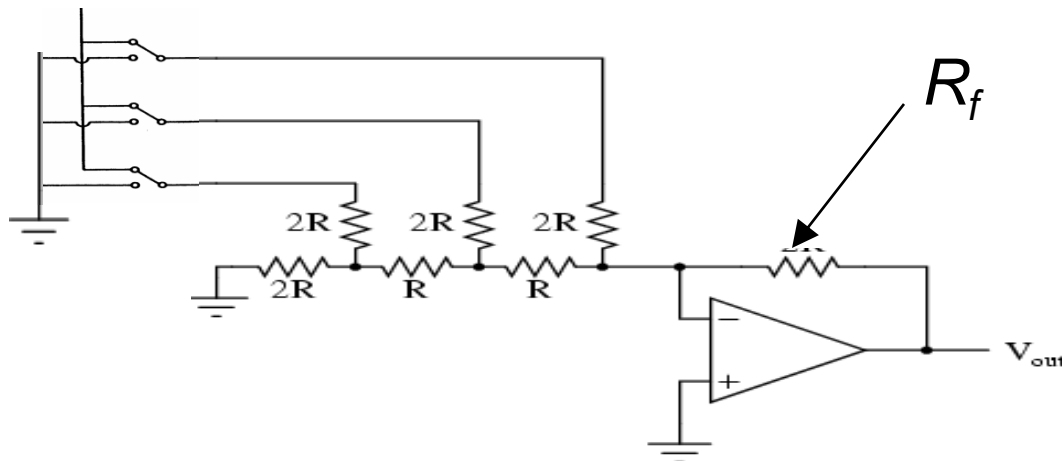

R-2R Ladder

- If $R_f = 6R$, V_{OUT} is same as Binary Weighted:

$$I = \frac{V_{REF}}{3R} \sum \frac{B_i}{2^{n-i}}$$

$$V_{OUT} = V_{REF} \sum \frac{B_i}{2^{n-i-1}}$$

- B_i = Value of Bit i

R-2R Ladder

■ Example:

□ Input = $(101)_2$

□ $V_{REF} = 10 \text{ V}$


□ $R = 2 \Omega$

□ $R_f = 2R$

$$I_0 = \frac{-V_{REF}}{2R + 2R \parallel 2R} = \frac{V_{REF}}{3R} = -1.67 \text{ mA}$$

$$I_{op-amp} = \frac{I_0}{8} + \frac{I_0}{2} = -1.04 \text{ mA}$$
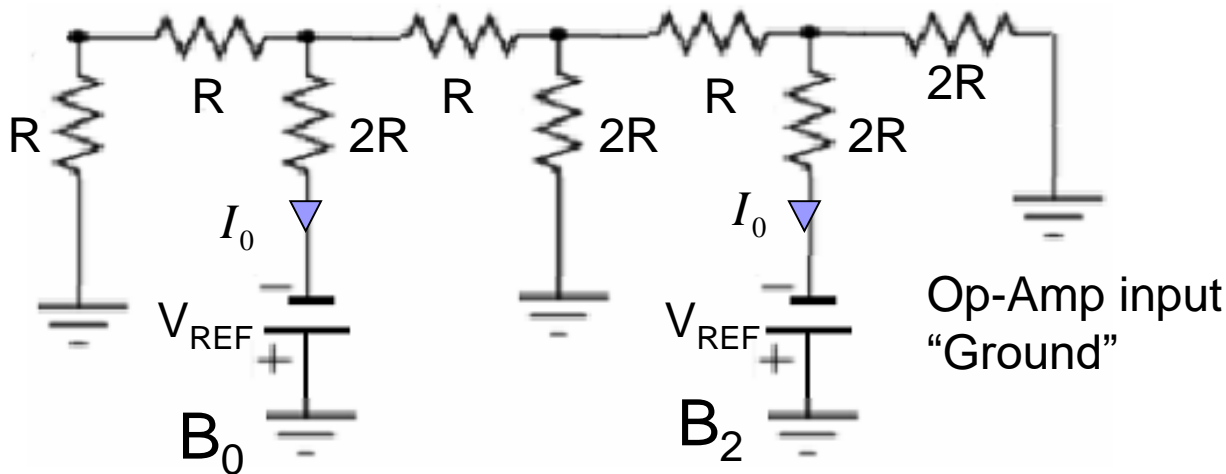
$$V_{OUT} = -I_{op-amp} R_f = 4.17 \text{ V}$$



Pros & Cons

	Binary Weighted	R-2R
Pros	Easily understood	Only 2 resistor values Easier implementation Easier to manufacture Faster response time
Cons	Limited to ~ 8 bits Large # of resistors Susceptible to noise Expensive Greater Error	More confusing analysis



Digital to Analog Converters

- Performance Specifications
- Common Applications



Digital to Analog Converters

-Performance Specifications

- Resolution
- Reference Voltages
- Settling Time
- Linearity
- Speed
- Errors

- Resolution: is the amount of variance in output voltage for every change of the LSB in the digital input.
- How closely can we approximate the desired output signal(Higher Res. = finer detail=smaller Voltage divisions)
- A common DAC has a 8 - 12 bit Resolution


$$\text{Resolution} = V_{LSB} = \frac{V_{\text{Ref}}}{2^N} \quad N = \text{Number of bits}$$

Digital to Analog Converters


-Performance Specifications

-Resolution

Poor Resolution(1 bit)

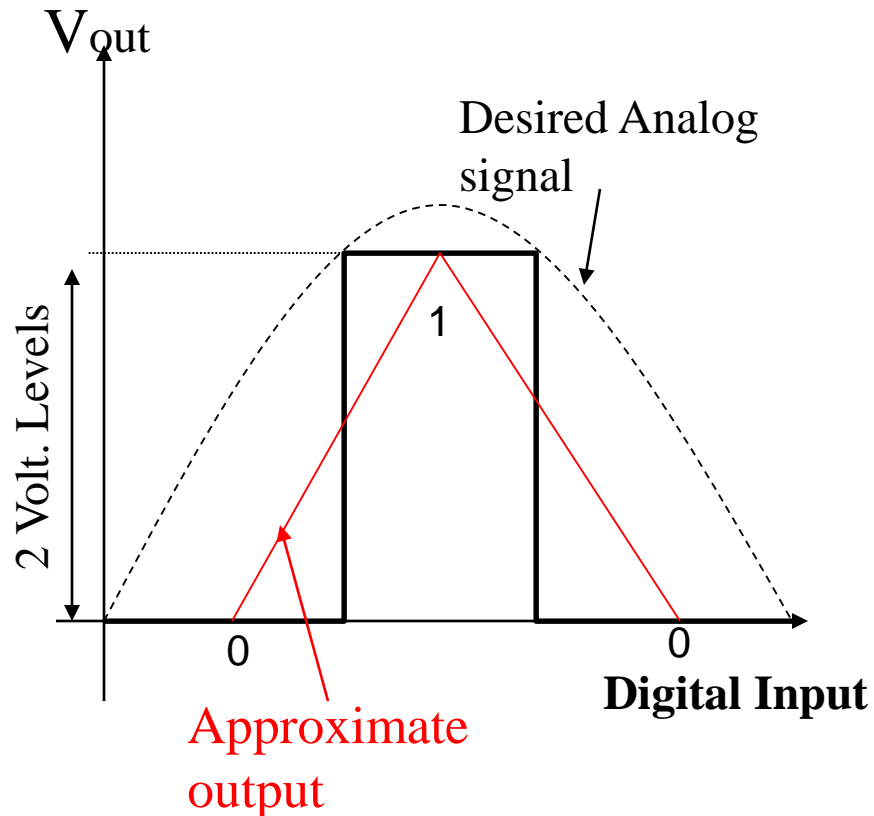

Better Resolution(3 bit)

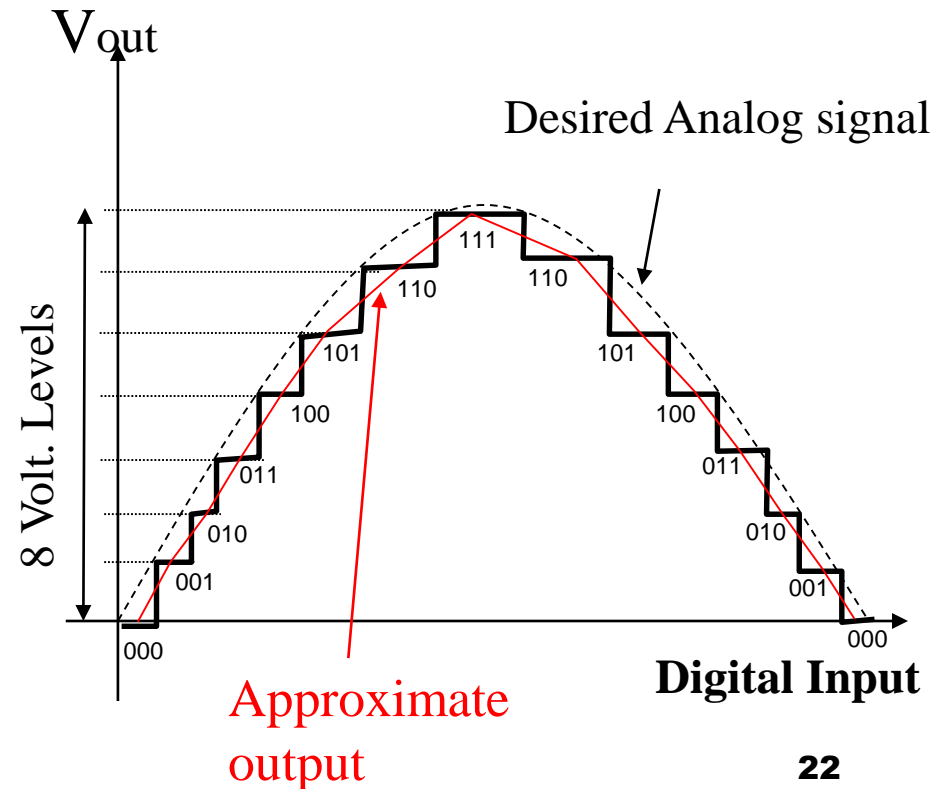

Digital to Analog Converters

-Performance Specifications

-Reference Voltage


- Reference Voltage: A specified voltage used to determine how each digital input will be assigned to each voltage division.
- Types:
 - Non-multiplier: internal, fixed, and defined by manufacturer
 - Multiplier: external, variable, user specified

Digital to Analog Converters


-Performance Specifications

-Reference Voltage

Non-Multiplier: ($V_{ref} = C$)

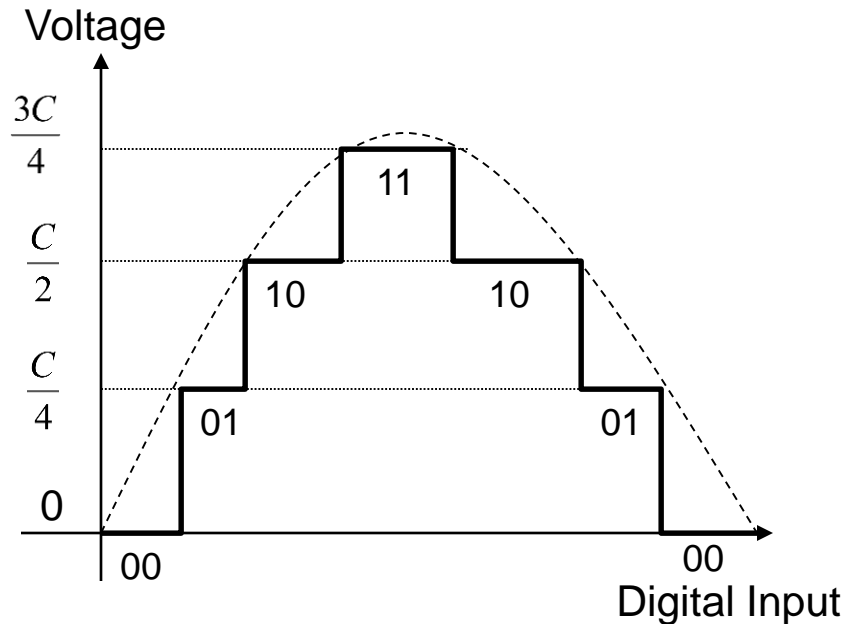

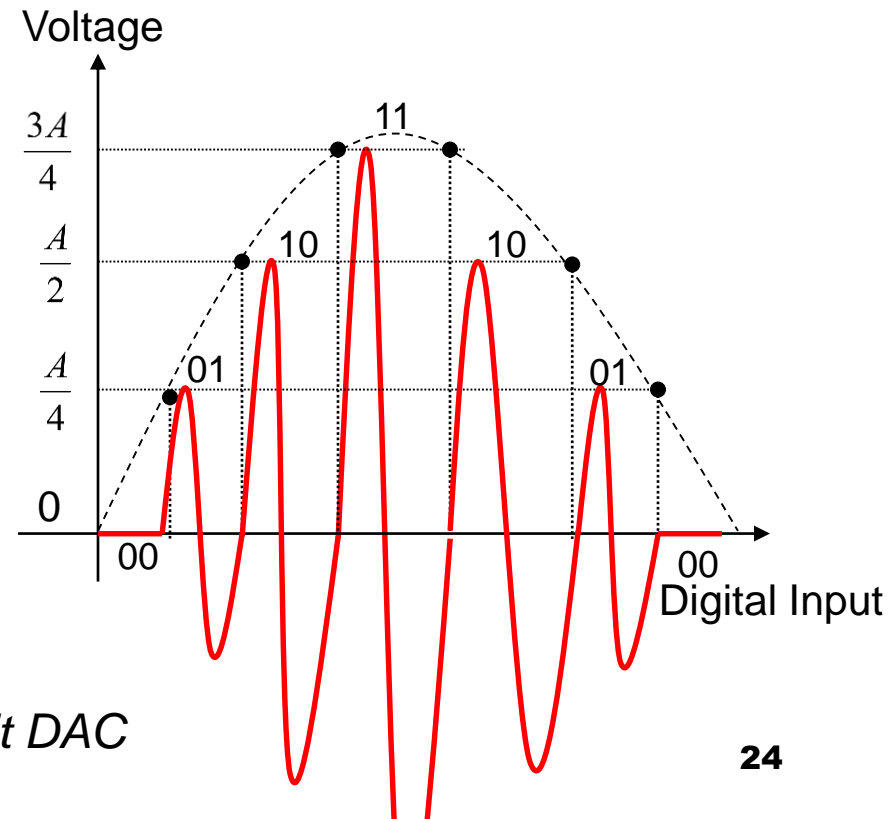Multiplier: ($V_{ref} = A \sin(\omega t)$)



Assume 2 bit DAC

Digital to Analog Converters

-Performance Specifications


-Settling Time

- Settling Time: The time required for the input signal voltage to settle to the expected output voltage (within $\pm V_{\text{LSB}}$).
- Any change in the input state will not be reflected in the output state immediately. There is a time lag, between the two events.

Digital to Analog Converters

-Performance Specifications

-Settling Time

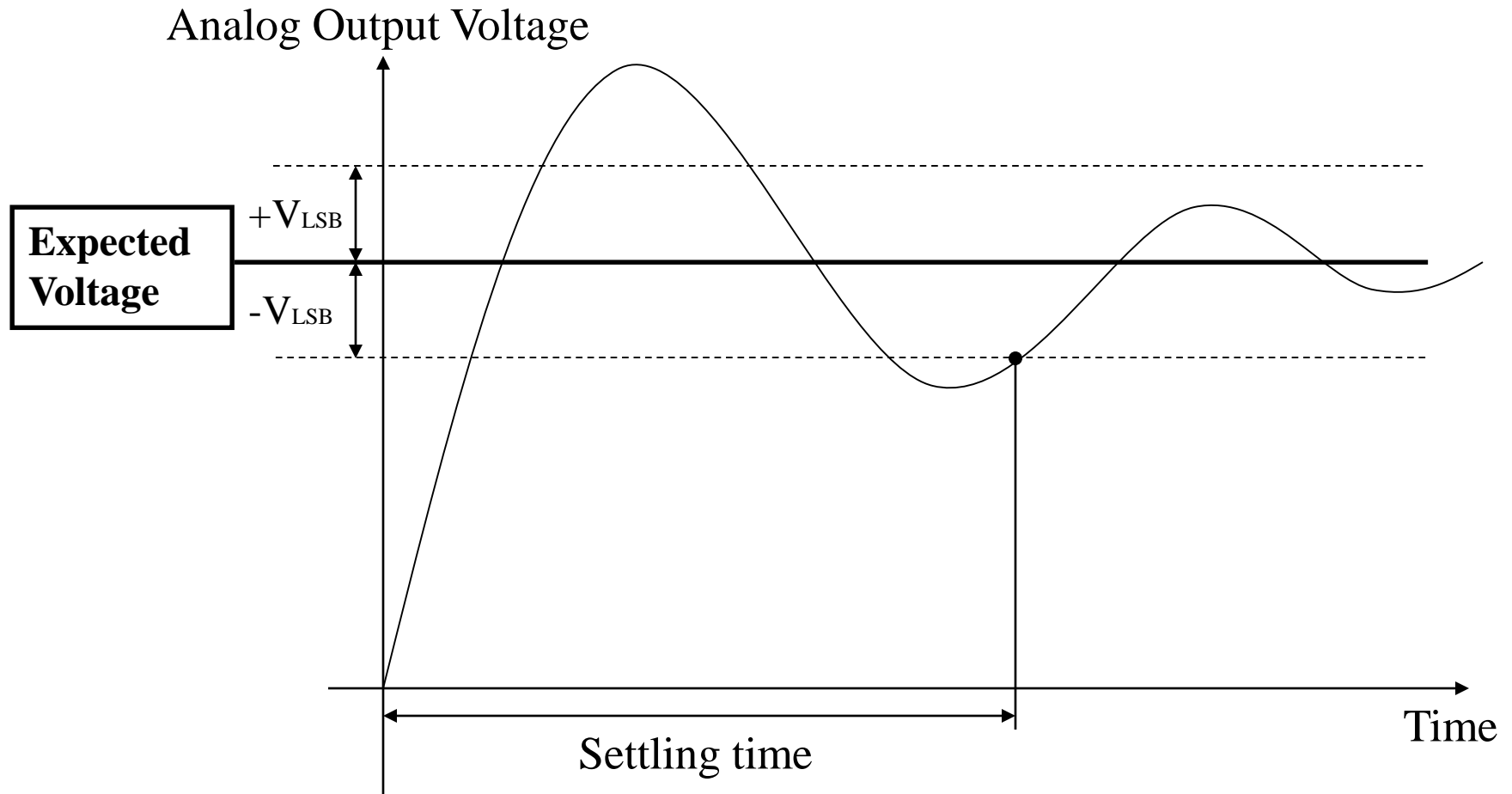

Digital to Analog Converters

-Performance Specifications

-Linearity


- Linearity: is the difference between the desired analog output and the actual output over the full range of expected values.
- Ideally, a DAC should produce a linear relationship between a digital input and the analog output, this is not always the case.

Digital to Analog Converters

-Performance Specifications


-Linearity

Linearity(Ideal Case)

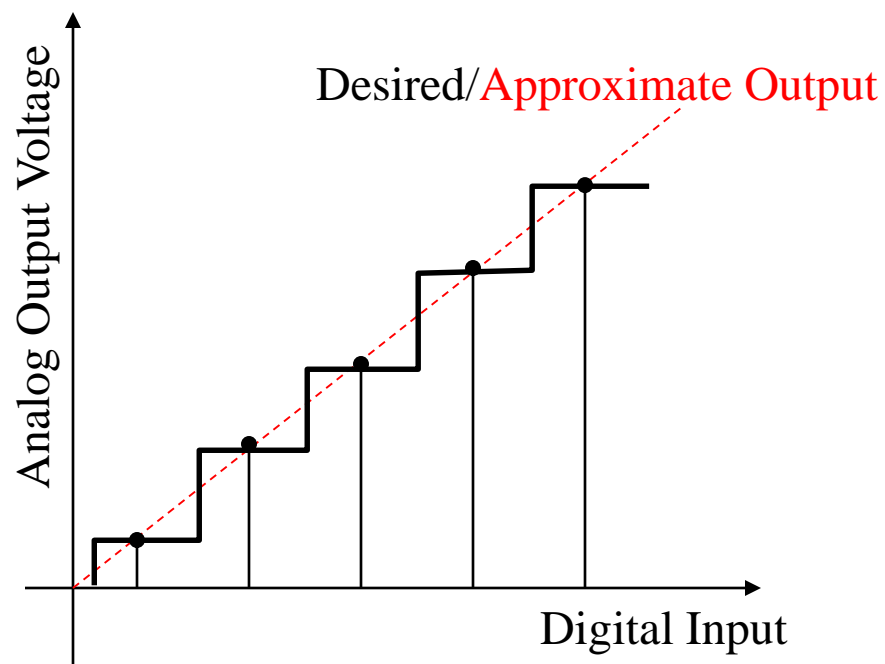

Perfect Agreement

NON-Linearity(Real World)

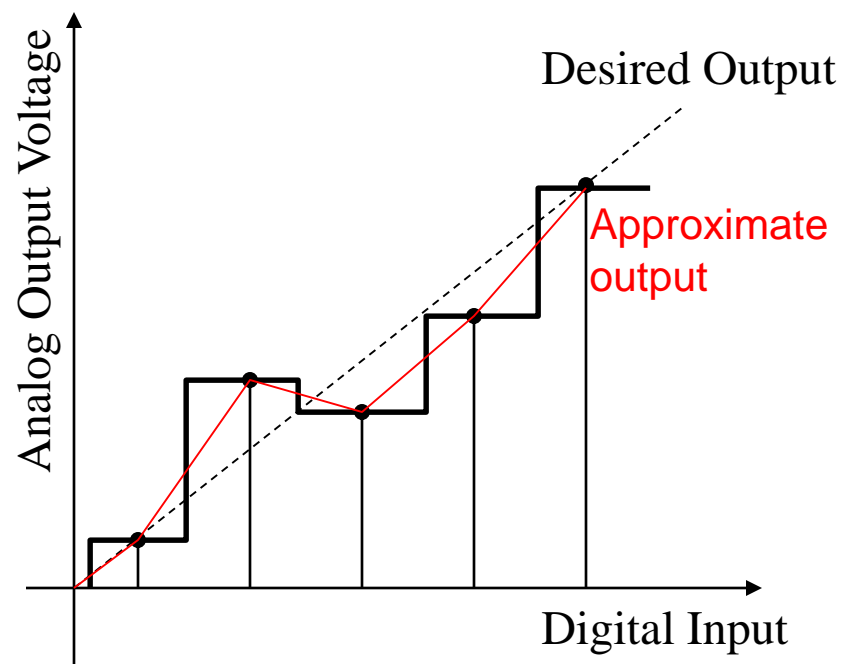

Miss-alignment

Digital to Analog Converters

-Performance Specifications

-Speed

- Speed: Rate of conversion of a single digital input to its analog equivalent
- Conversion Rate
 - Depends on clock speed of input signal
 - Depends on settling time of converter



Digital to Analog Converters

-Performance Specifications

-Errors


- Non-linearity
 - Differential
 - Integral
- Gain
- Offset
- Non-monotonicity

Digital to Analog Converters

-Performance Specifications

-Errors: Differential Non-Linearity

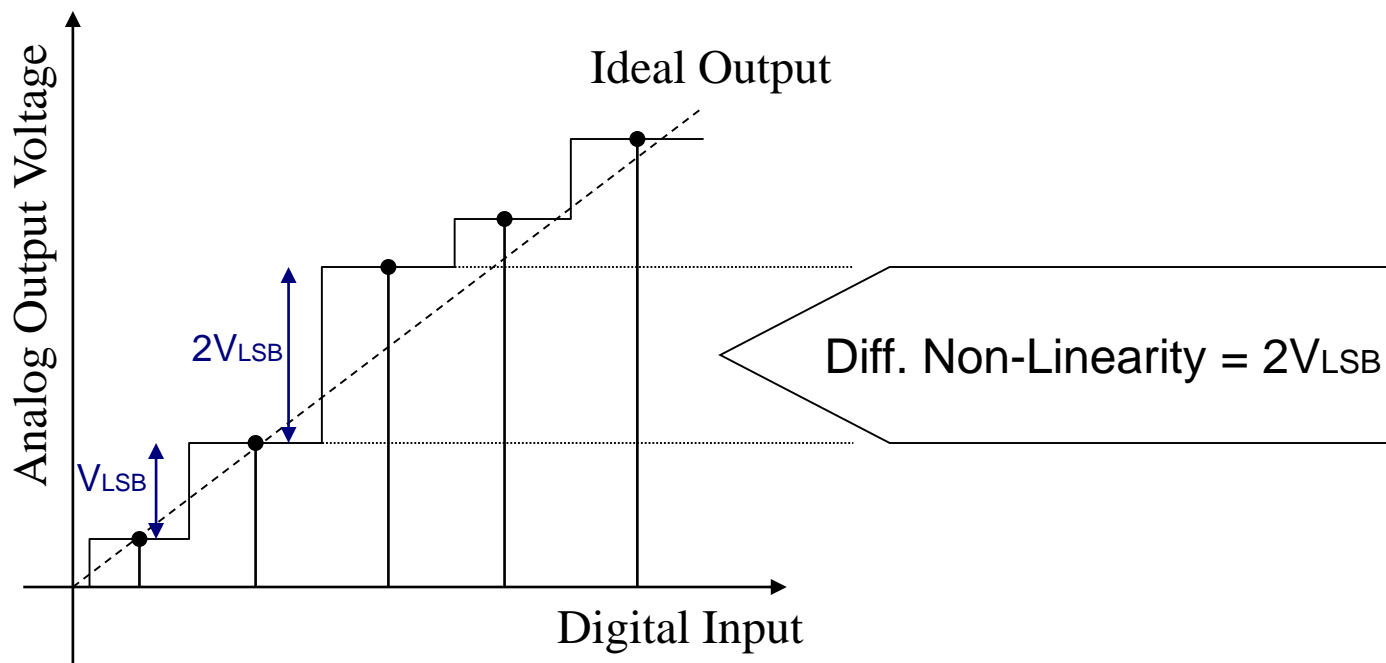- Differential Non-Linearity: Difference in voltage step size from the previous DAC output (Ideally All DLN's = $1 V_{\text{LSB}}$)




Digital to Analog Converters

-Performance Specifications

-Errors: Integral Non-Linearity

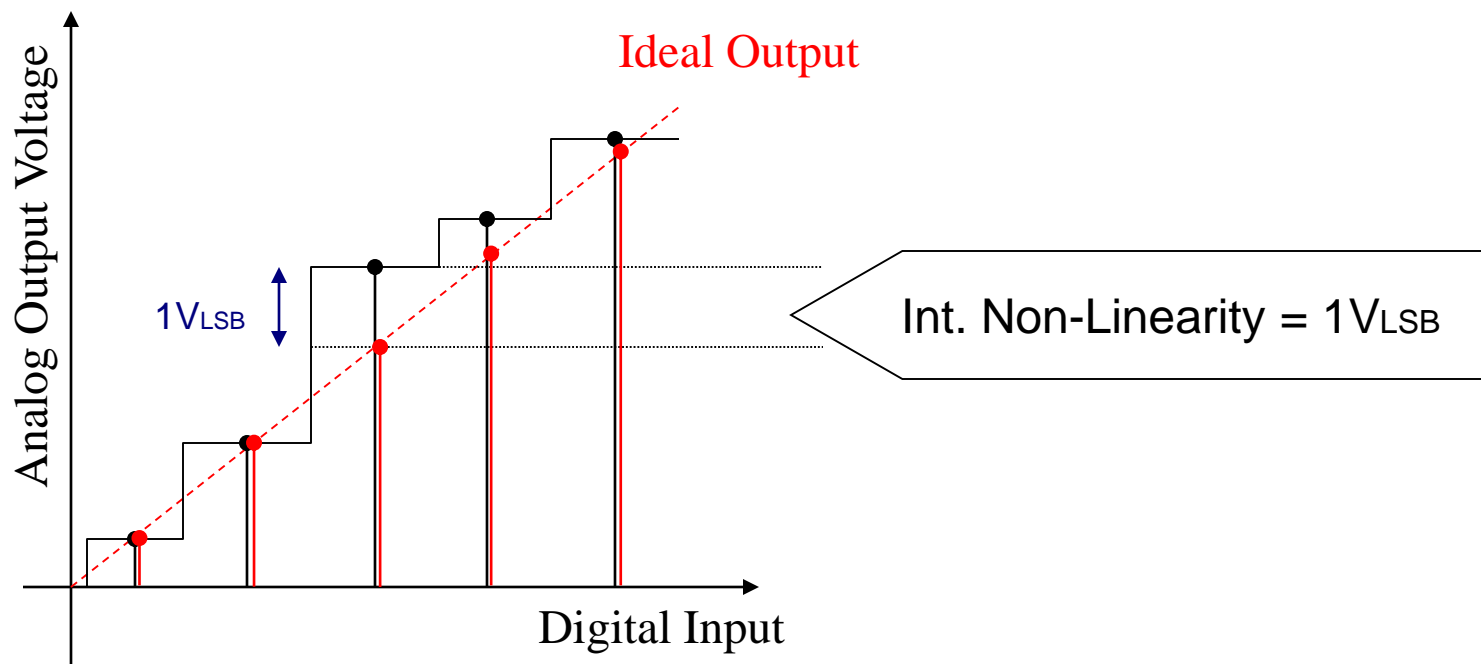- Integral Non-Linearity: Deviation of the actual DAC output from the ideal (Ideally all INL's = 0)



Digital to Analog Converters


-Performance Specifications

-Errors: Gain

- Gain Error: Difference in slope of the ideal curve and the actual DAC output

High Gain Error: Actual slope greater than ideal

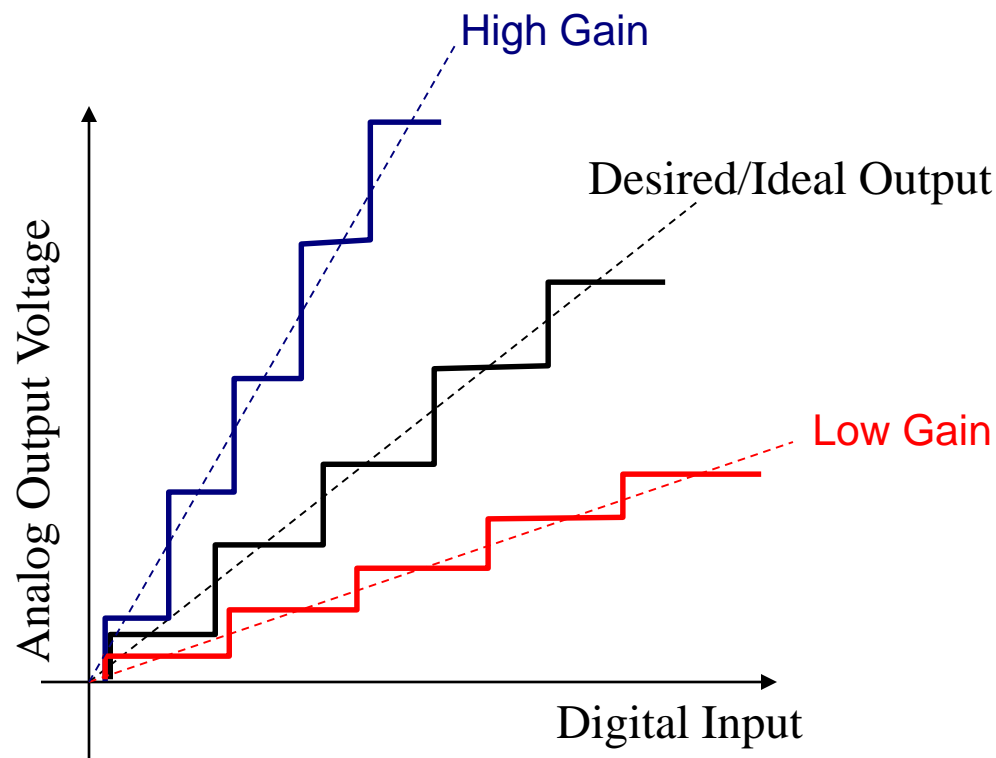Low Gain Error: Actual slope less than ideal




Digital to Analog Converters

-Performance Specifications

-Errors: Offset

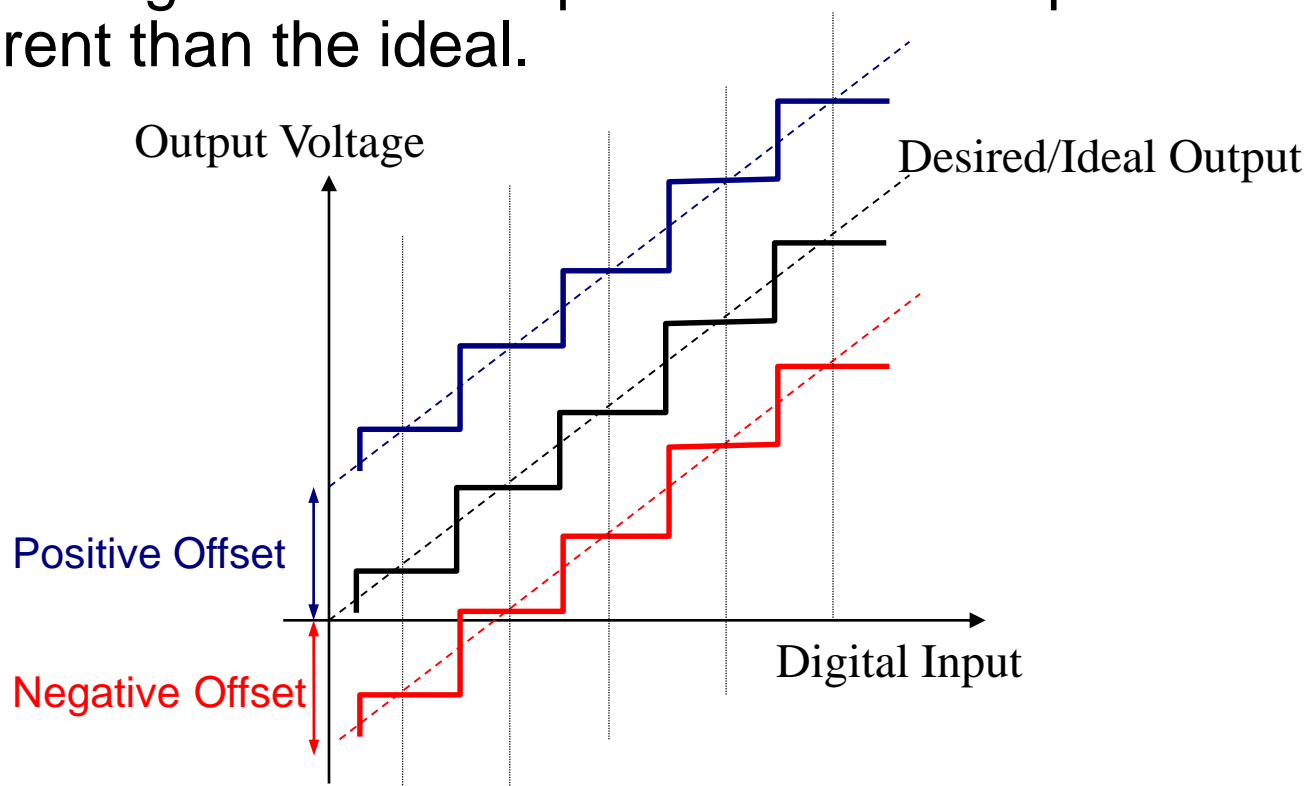- Offset Error: A constant voltage difference between the ideal DAC output and the actual.
- The voltage axis intercept of the DAC output curve is different than the ideal.




Digital to Analog Converters

-Performance Specifications

-Errors: Non-Monotonicity

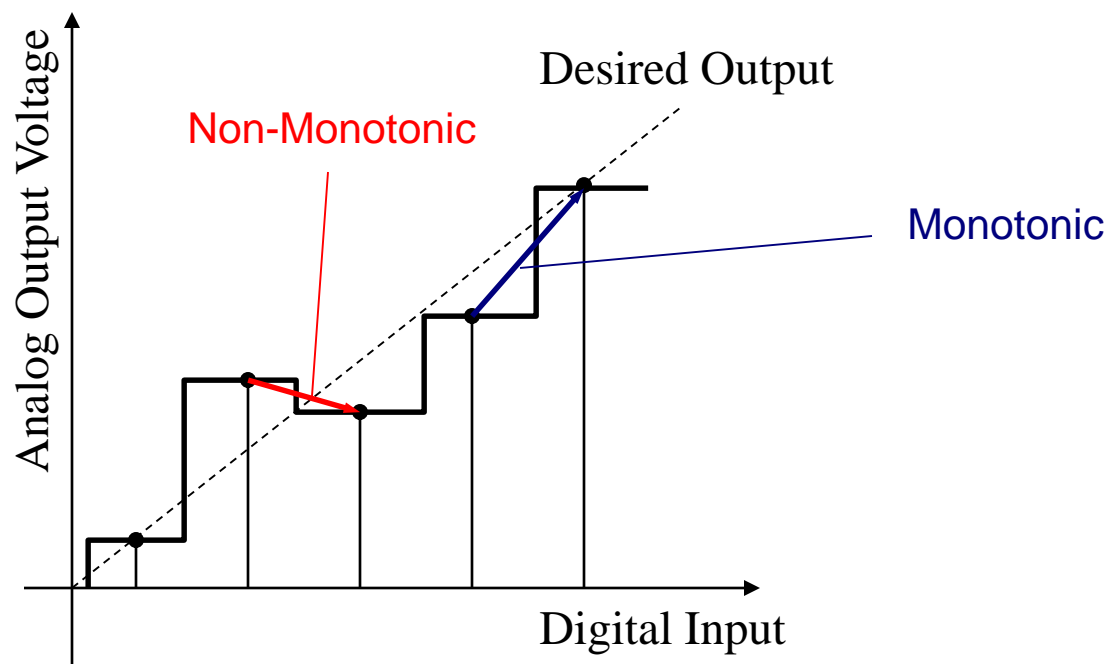- Non-Monotonic: A decrease in output voltage with an increase in the digital input





Digital to Analog Converters

-Common Applications


- Generic use
- Circuit Components
- Digital Audio
- Function Generators/Oscilloscopes
- Motor Controllers

Digital to Analog Converters

-Common Applications

-Generic

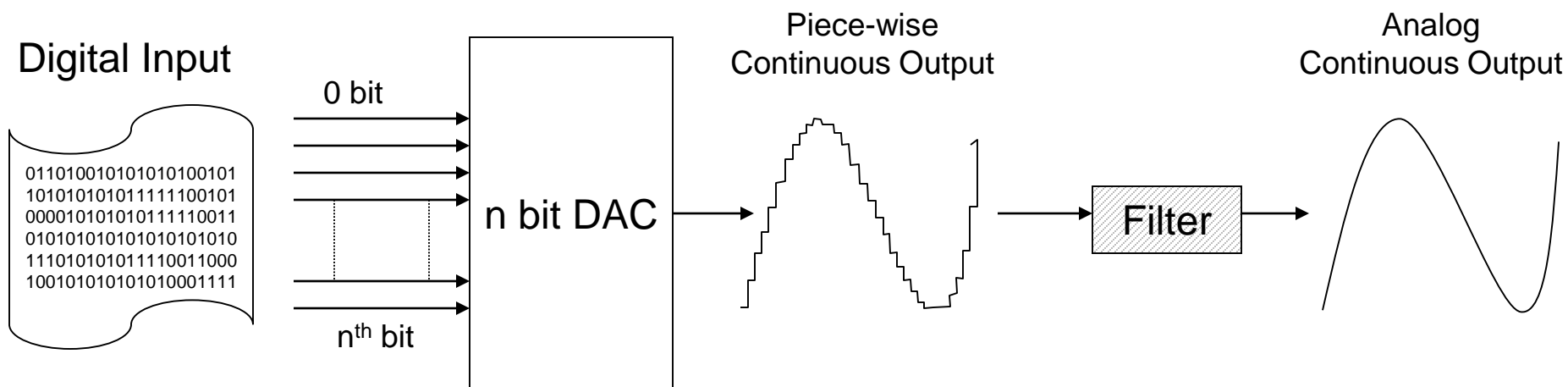- Used when a continuous analog signal is required.
- Signal from DAC can be smoothed by a Low pass filter





Digital to Analog Converters

-Common Applications

-Circuit Components

- Voltage controlled Amplifier
 - digital input, External Reference Voltage as control

- Digitally operated attenuator
 - External Reference Voltage as input, digital control

- Programmable Filters
 - Digitally controlled cutoff frequencies

Digital to Analog Converters

-Common Applications

-Digital Audio

- CD Players
- MP3 Players
- Digital Telephone/Answering Machines



1. <http://electronics.howstuffworks.com/cd.htm>

2. http://accessories.us.dell.com/sna/sna.aspx?c=us&cs=19&l=en&s=dhs&~topic=odg_dj

3. http://www.toshiba.com/taistsd/pages/prd_dtc_digphones.html

Digital to Analog Converters

-Common Applications

-Function Generators

■ Digital Oscilloscopes

- ☐ Digital Input
- ☐ Analog Output

■ Signal Generators

- ☐ Sine wave generation
- ☐ Square wave generation
- ☐ Triangle wave generation
- ☐ Random noise generation

1



2



1. http://www.electrorent.com/products/search/General_Purpose_Oscilloscopes.html

2. http://www.bkprecision.com/power_supplies_supply_generators.htm

Digital to Analog Converters

-Common Applications

-Motor Controllers

- Cruise Control
- Valve Control
- Motor Control



1. <http://auto.howstuffworks.com/cruise-control.htm>
2. <http://www.emersonprocess.com/fisher/products/fieldvue/dvc/>
3. <http://www.thermionics.com/smc.htm>