

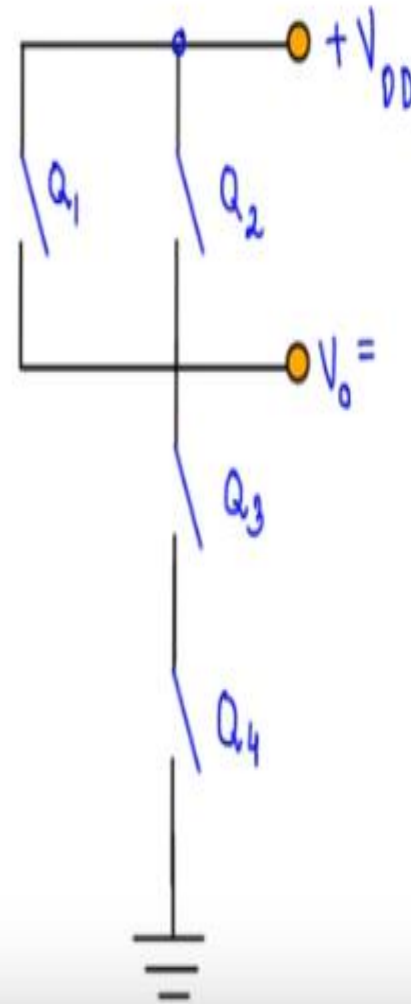
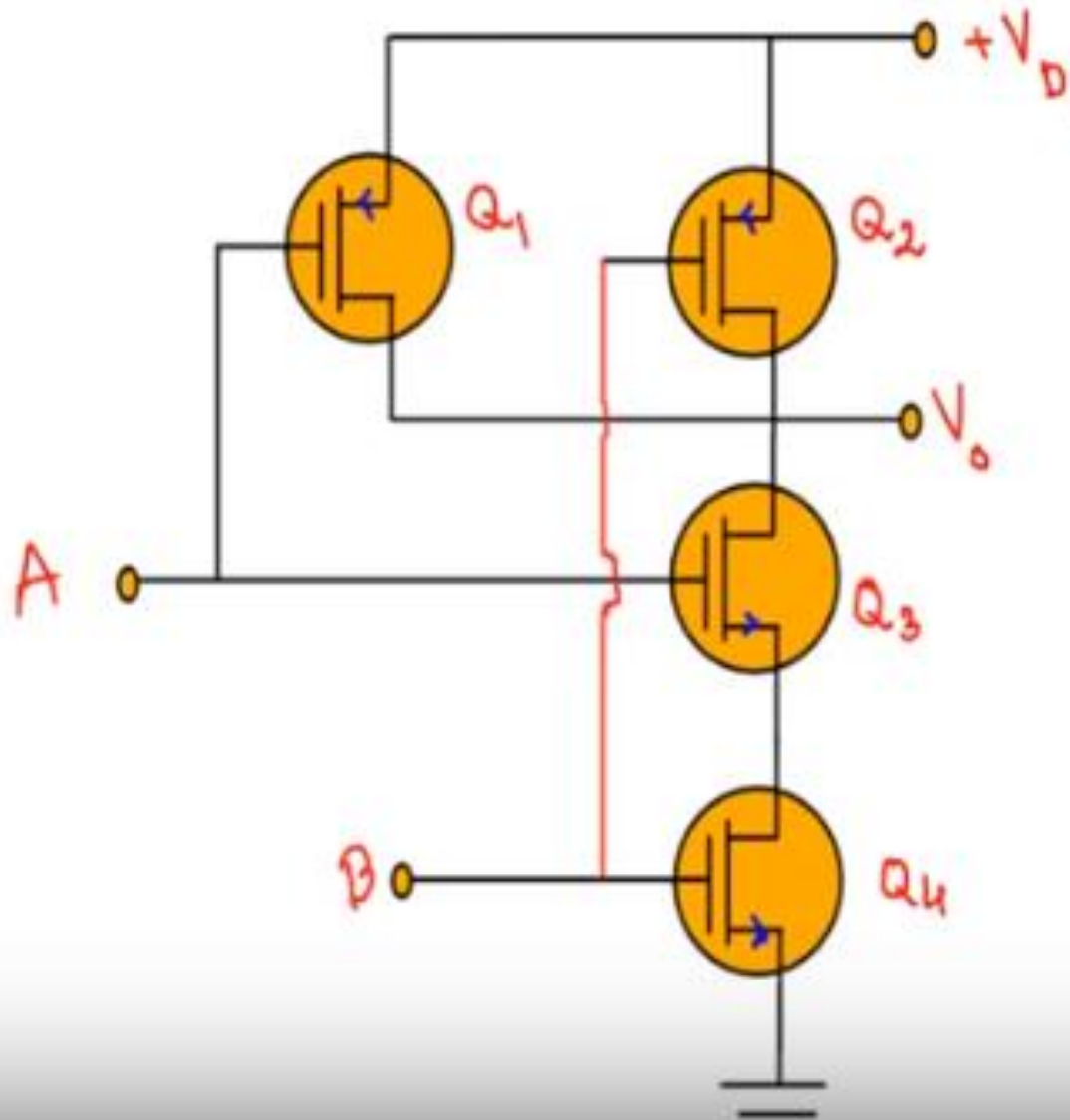


CMOS NAND

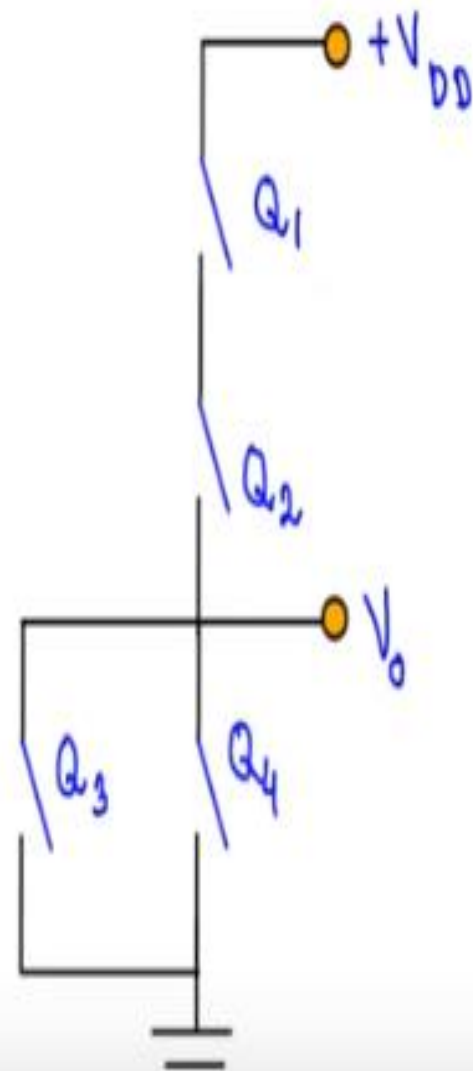

A	B	Q_1	Q_2	Q_3	Q_4	V_o
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

CMOS NOR GATE

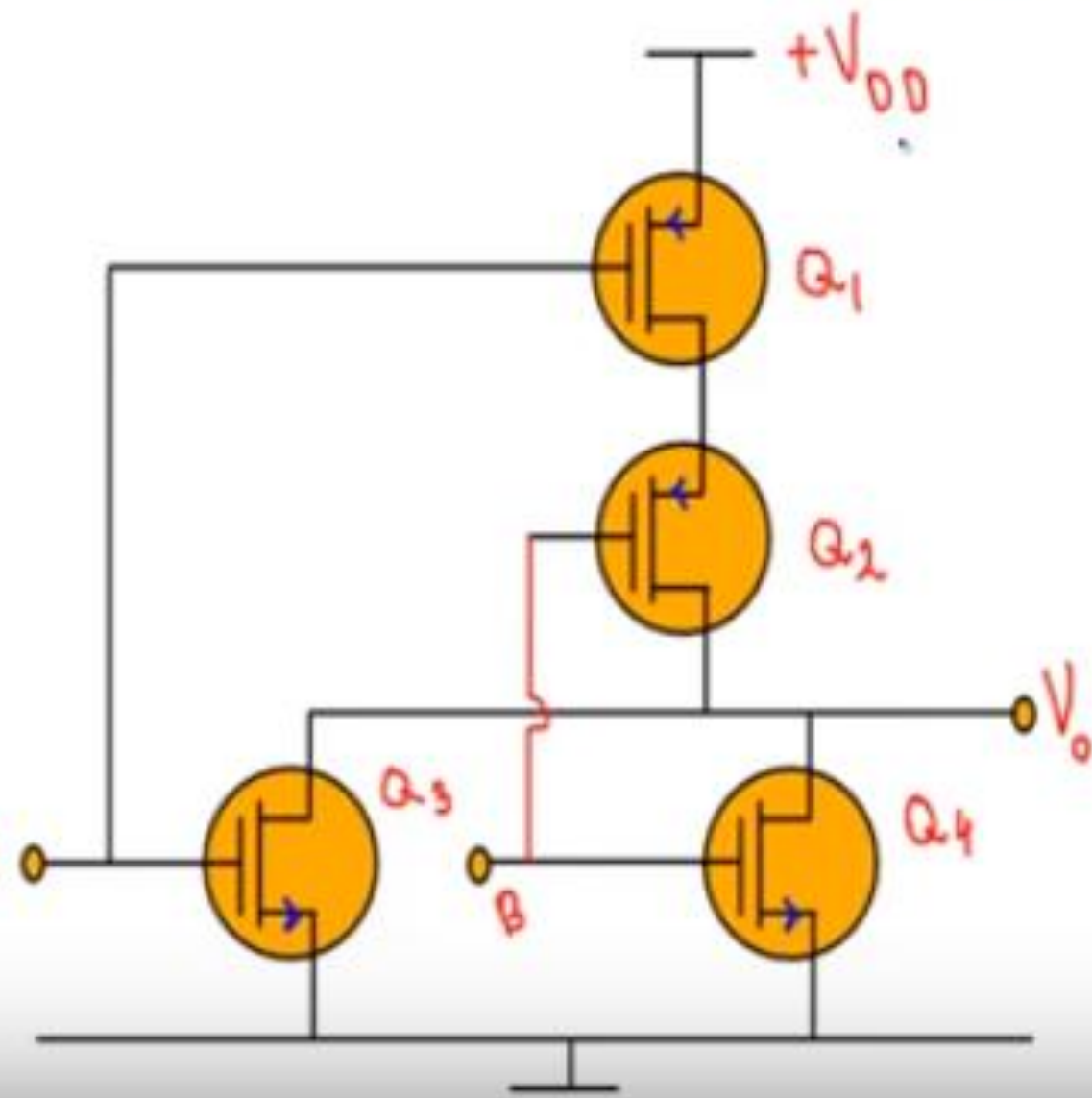

A	B	Q_1	Q_2	Q_3	Q_4	V_o
0	0	on	on	off	off	1
0	1	on	off	off	on	0
1	0	off	on	on	off	0
1	1	off	off	on	on	0

Multivibrators

- A multivibrator is used to implement simple **two-state systems** such as oscillators, timers and flip-flops.
- Three types:
 - **Astable** – neither state is stable.
Applications: oscillator, etc.
 - **Monostable** - one of the states is stable, but the other is not;
Applications: timer, etc.
 - **Bistable** – it remains in either state indefinitely.
Applications: flip-flop, etc.

Astable Multivibrator:

A multivibrator that generates square waveform without using any external triggering pulse is known as astable or free running multivibrator.


input

circuit



output

none


Astable
Multivibrator

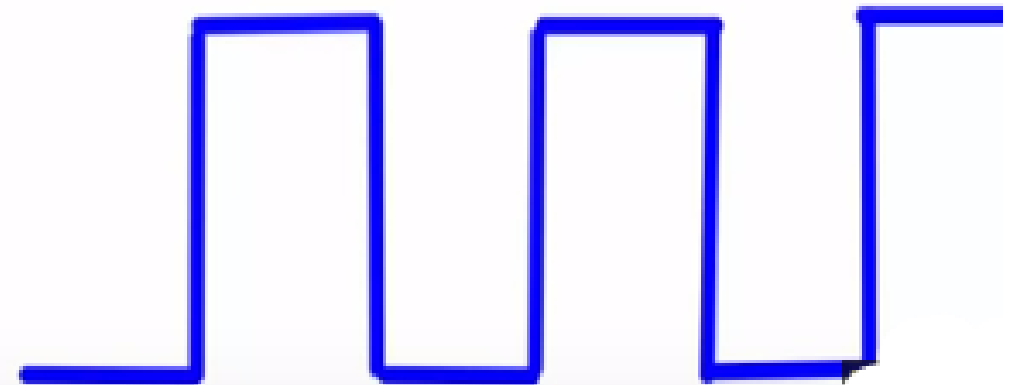

Astable Multivibrator

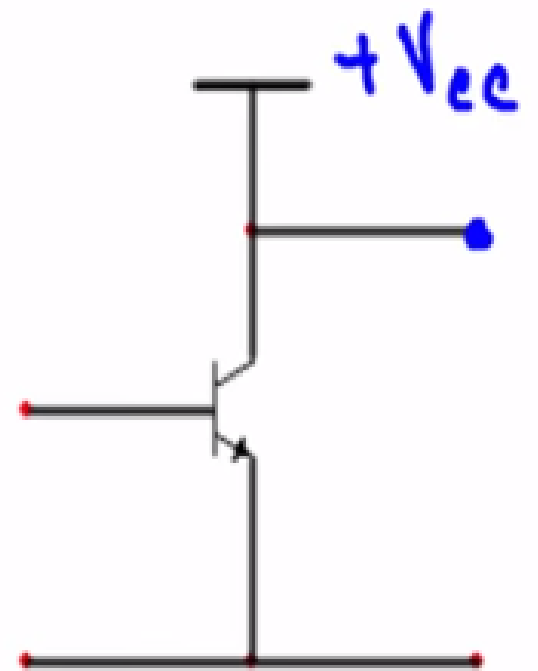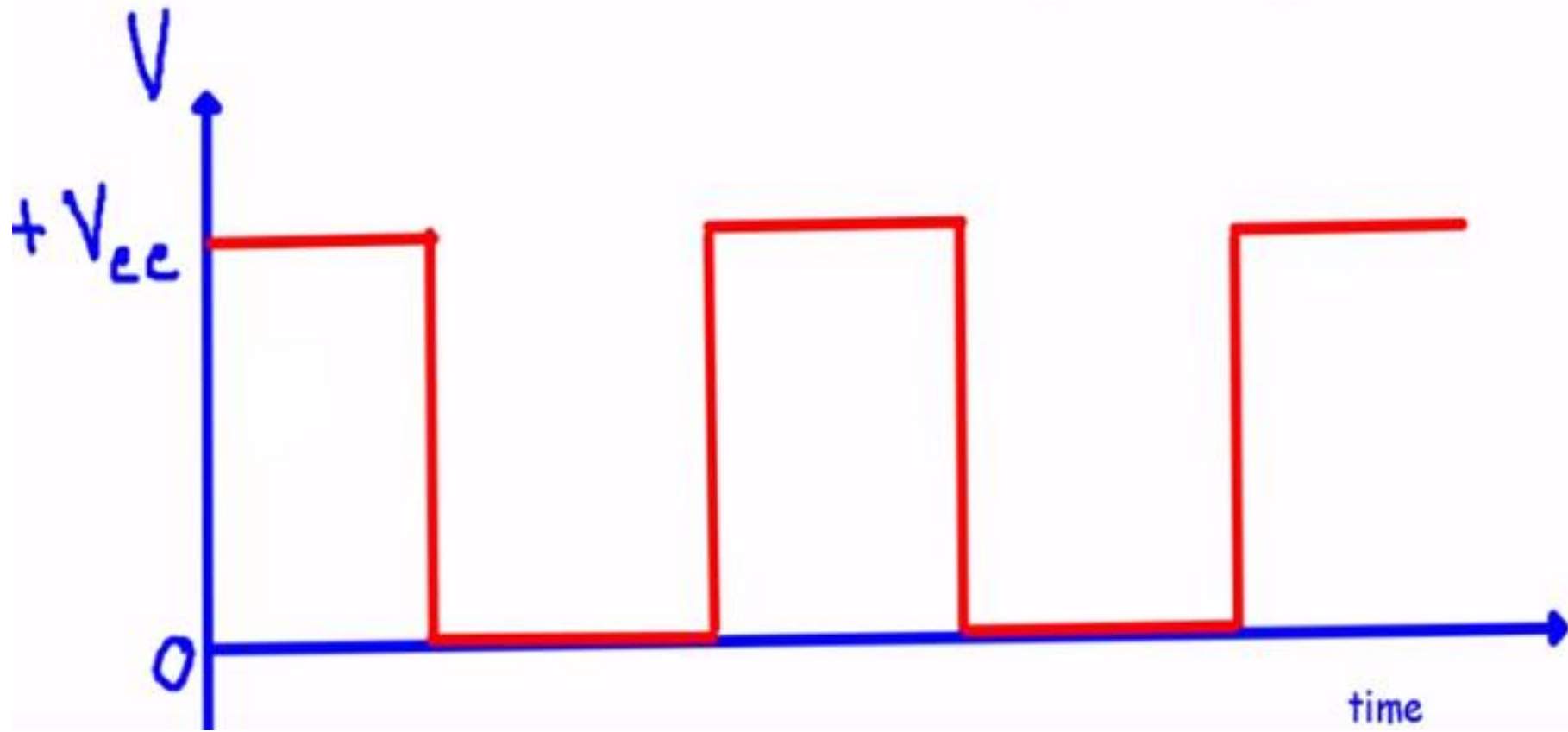

Astable Multivibrator

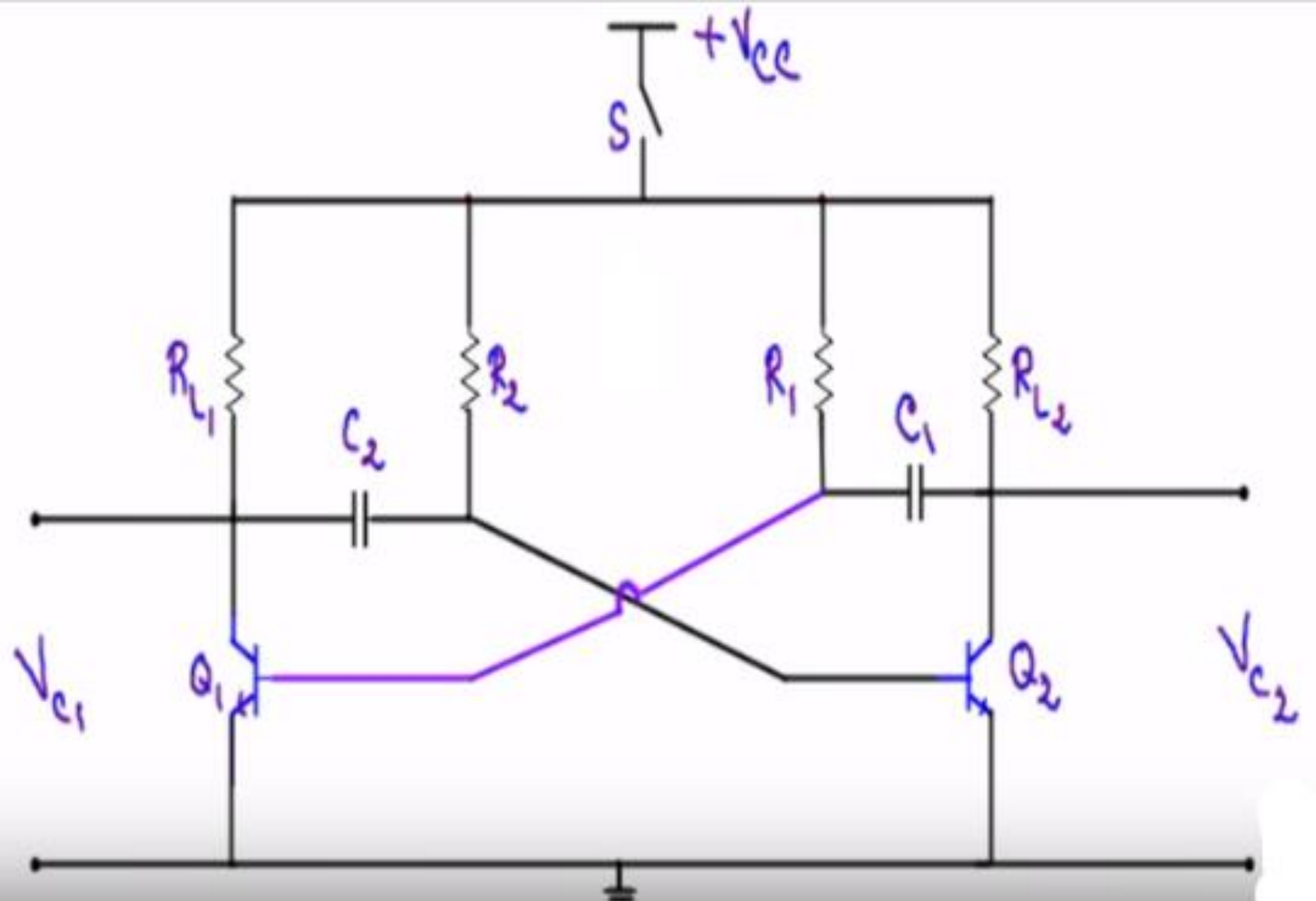

Astable Multivibrator

